




# CHAPTER ONE

## *Properties of Digital Integrated Ccts.*

*Digital Electronics.*
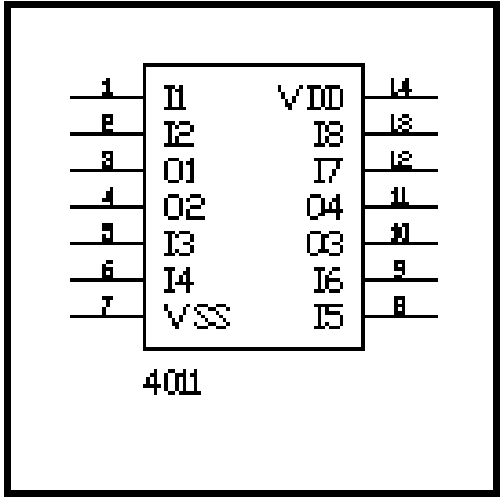  
# Basic Logic Operations

- AND
- NOT
- NAND
- OR
- NOR
- XOR
- XNOR



4 2-in AND



4 outputs with  
Two-input AND gates

# Basic Logic Operations

- **Combinational logic:**

Output depends only on present value of the input.

- **Sequential logic:**


Output depends on present/past value of the input.

# Basic Logic Operations



- The voltages/currents in digital logic circuits have two possible states (*according to positive voltage logic*) ✓:
  - Low voltage corresponds to a binary 0
  - High voltage corresponds to a binary 1
- *But according to negative voltage logic:*
  - Low voltage corresponds to a binary 1
  - High voltage corresponds to a binary 0

# Basic Building Blocks

- Inverter (NOT)

 

- Non-inverter (Buffer)

 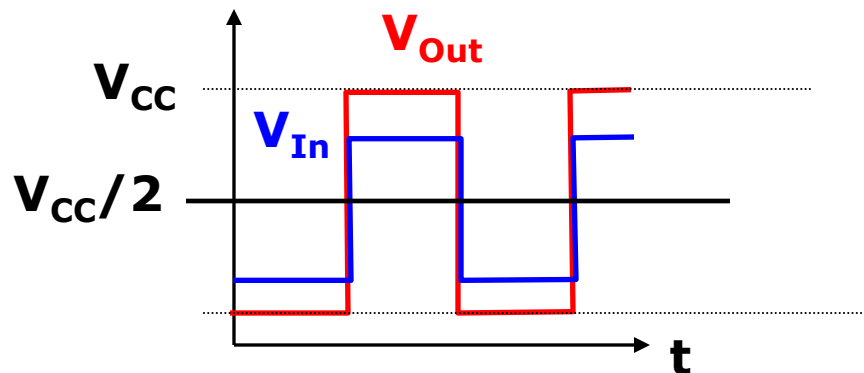

Used to regenerate voltage levels by making degraded high levels higher and degraded low levels lower

# Voltage Transfer Characteristics (VTC) of Inverters



- Ideal

- Practical

- 1  $V_{OH}$ : Output high voltage level
- 2  $V_{OL}$ : Output low voltage level
- 3  $V_{IL}$ : Max. Input voltage that provides high output voltage
- 4  $V_{IH}$ : Min. Input voltage that provides low output voltage
- 5  $V_M$ : Midpoint ( $V_{Out} = V_{In}$ ) ideally  $\sim V_{CC}/2$
- 6  $V_{LS}$ : Logic swing voltage.
- 7  $V_{TW}$ : Transition width, change in input to cause a change in output

The outputs of present inverter will be inputs to the next gate, "Low and High levels must be distinguishable"

$V_{OH} > V_{IH}$   
 $V_{OL} < V_{IL}$

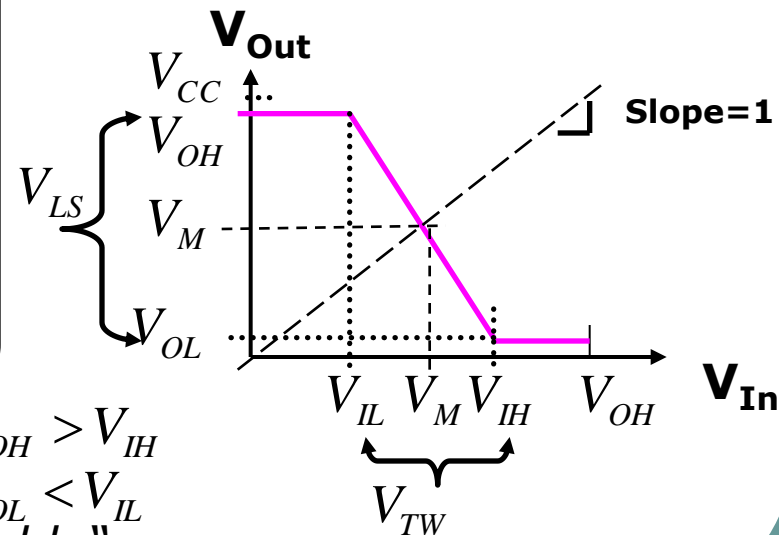 

# Voltage Transfer Characteristics (VTC) of Inverters

## ● Example

Assume  $V_{OH} = 4.3 \text{ V}$ ,  $V_{OL} = 0.2 \text{ V}$ ,  $V_{IL} = 0.7 \text{ V}$ ,  $V_{IH} = 0.9 \text{ V}$

Calculate  $V_{LS}$ ,  $V_{TW}$ , and  $V_M$

## ● Solution


$$V_{LS} = 4.1 \text{ V},$$
$$V_{TW} = 0.2 \text{ V},$$

$$Y - y_0 = \text{slope}(x - x_0)$$

$$Y - 4.3 = [(0.2 - 4.3) / (0.9 - 0.7)](x - 0.7)$$

$$Y = x \rightarrow y = 0.867 \text{ V}$$
 
$$\rightarrow V_M = 0.867 \text{ V} \quad \text{far from } V_{CC}/2$$



# Noise in Digital Ccts.

- **Noise:** Fluctuations (variations, degradations) of the steady state voltage levels

- **Noise margins:**

- Low noise margin
- High noise margin

$$V_{NML} = V_{IL} - V_{OL}$$

$$V_{NMH} = V_{OH} - V_{IH}$$

Safety margins  
(have to be positive)

- **Noise Sensitivities:**

- Low noise sensitivity
- High noise sensitivity

$$V_{NSL} = V_M - V_{OL}$$

$$V_{NSH} = V_{OH} - V_M$$

- **Noise Immunities** (ability of a gate to reject noise)

- Low noise immunity


$$V_{NIL} = V_{NSL} / V_{LS}$$

- High noise immunity

$$V_{NIH} = V_{NSH} / V_{LS}$$




# Fan-In and Fan-Out

 

- Fan-In: (less concern)  
Number of inputs of a gate.
- Fan-Out:  
Number of outputs of a gate.

# Maximum Fan-Out of a Digital Gate

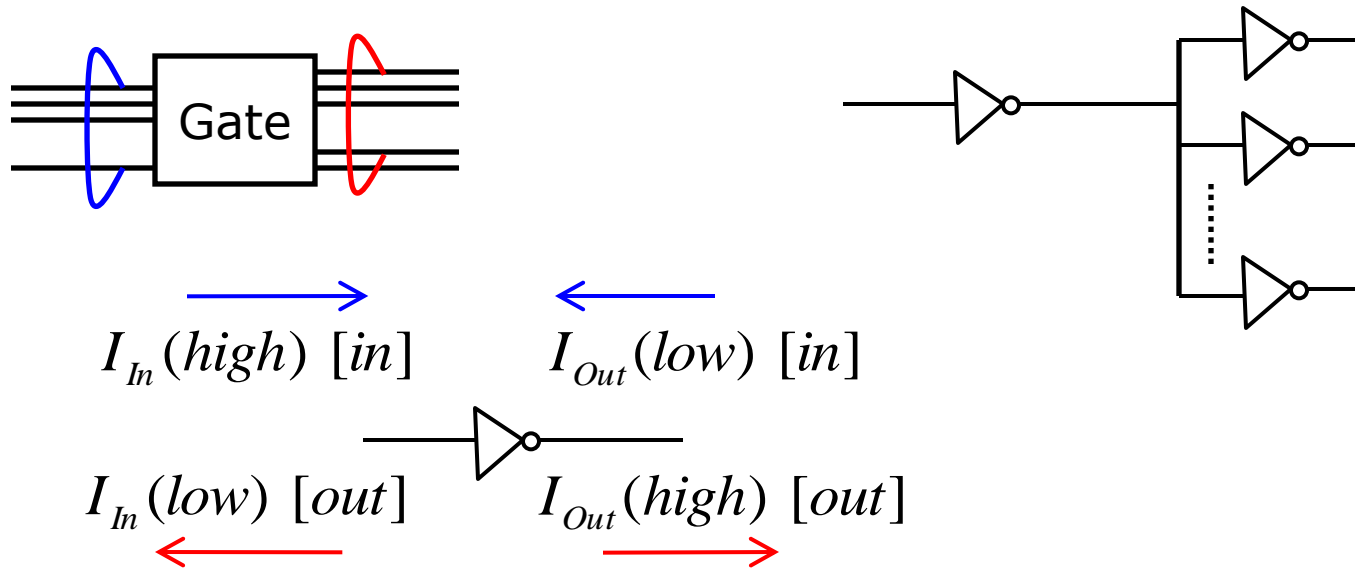


- Maximum Fan-out =  $\min\{N_{low}, N_{high}\}$

$$N_{low} = \frac{I_{Out}(low)}{I_{In}(low)}$$

$$N_{high} = \frac{I_{Out}(high)}{I_{In}(high)}$$

# Maximum Fan-Out of a Digital Gate

 

## ● Example

Assume  $I_{In}(high) = 98.9\mu A$      $I_{In}(low) = 2.43mA$   
 $I_{Out}(high) = 71.4mA$      $I_{Out}(low) = 54.3mA$

**Calculate the maximum fan-out.**


## ● Solution

$$N_{low} = \frac{I_{Out}(low)}{I_{In}(low)} = \frac{54.3}{2.43} = 22.3$$

$$N_{high} = \frac{I_{Out}(high)}{I_{In}(high)} = \frac{71.4}{0.0989} = 721.9$$



**maximum fan-out= 22**

 


Rounded to the nearest lowest integer
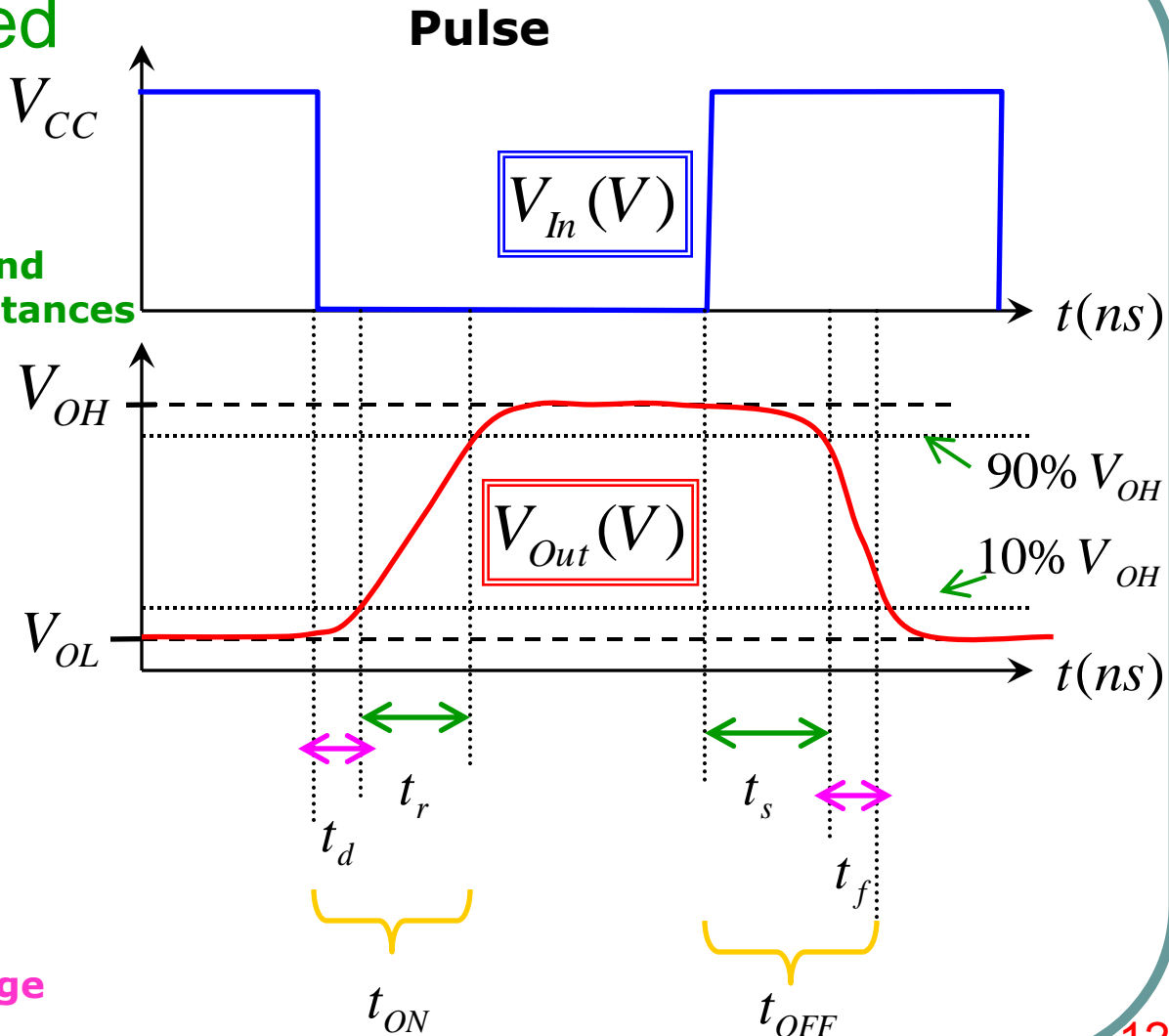
# Transient Characteristics

- Switching speed

Associated with charging and discharging the load capacitances



$t_d$  = delay time

$t_r$  = rise time

$t_s$  = storage time

$t_f$  = fall time

$t_{ON}$  = turn - on time =  $t_d + t_r$

$t_{OFF}$  = turn - off time =  $t_s + t_f$


Associated with stored charge of pn junction

# Transient Characteristics

- Switching voltage high  $\Leftrightarrow$  low requires a finite amount of time, i.e., the output does not respond immediately (delay).
- *Propagation delay time (PDT)*: is the time interval between the application of an input and the response of the resulting output.
- In **BJTs**, PDT is caused by the time required to store and remove the charge from the **base region**.
- In **MOSFETs**, PDT is caused by the **metal oxide capacitance**

# Transient Characteristics

- Propagation delays

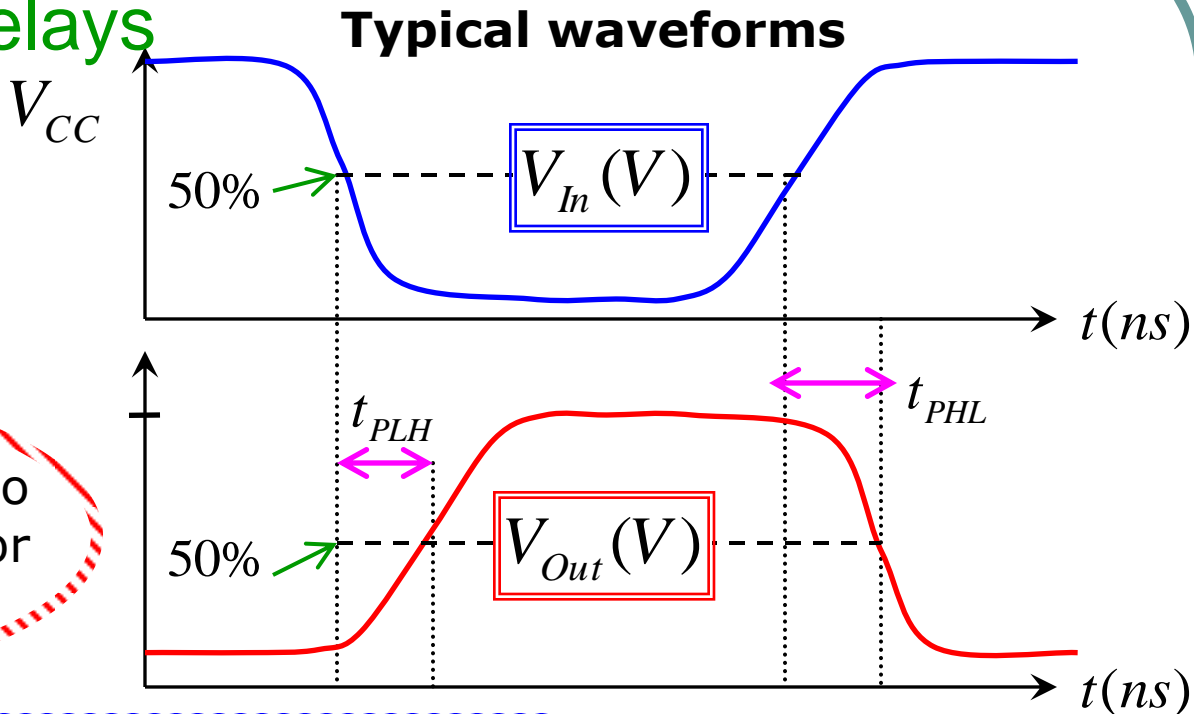


The 50% points are used to define the time required for the output to respond

$t_{PLH}$  = refers to low - to - high transition of the output

$t_{PHL}$  = refers to high - to - low transition of the output

$$t_p (avg) = \frac{t_{PLH} + t_{PHL}}{2}$$

# Transient Characteristics

 

- Example

See example **1.5** on page 9

# Transient Characteristics



- Power dissipation:

- An ideal gate has a single power supply
- The power dissipated equals the power supplied
- The dissipated power in logic high and logic low states may differ

$$P_{CC}(avg) = \frac{P_{CC}(OH) + P_{CC}(OL)}{2}$$
$$= \left( \frac{I_{CC}(OH) + I_{CC}(OL)}{2} \right) V_{CC}$$

- Some gates have two power supplies (+ & -)
  
$$P_{DISS}(avg) = P_{CC}(avg) + P_{EE}(avg)$$
$$= \left( \frac{I_{CC}(OH) + I_{CC}(OL)}{2} \right) V_{CC} + \left( \frac{I_{EE}(OH) + I_{EE}(OL)}{2} \right) V_{EE}$$





# Transient Characteristics

- **Power-Delay product (*speed-power product*):**
  - Low power dissipation and short propagation delay are desirable for digital ICs.
  - But, faster propagation delay times are achieved at the cost of increased power dissipation.
  - As a figure of merit, power-delay product is defined as
$$PD = P_{DISS} (avg) \times t_p (avg) \quad [J]: \text{joules}$$
  - The smaller the PD is, the more ideal the gate is.  
*Ideally PD=0 J.*

# Assignment # 1

- HW #1: Solve Problems: 1.1, 1.5, 1.12, 1.22, and 1.24