


CHAPTER TWENTY FOUR

CMOS Combinational Logic Circuits


Introduction

This chapter presents the structure of multi-input CMOS gates such as NANDs, NORs, AND-OR-Inverts (AOIs)

CMOS Inverter

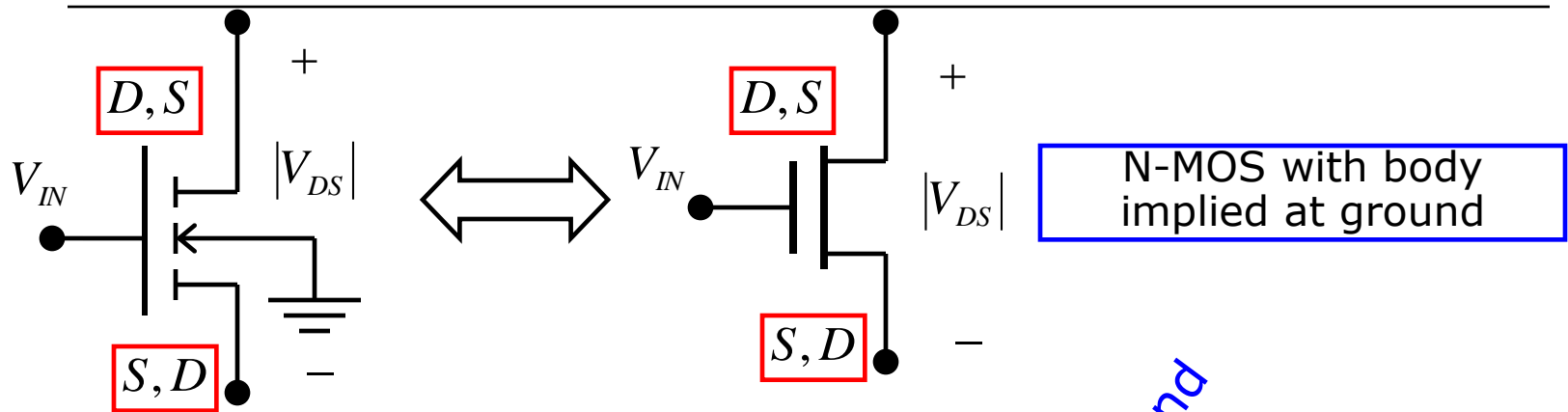

Shorthand symbols

 

CMOS Inverter


When V_{IN} is low, i.e. $V_{IN} = V_{GS} < V_{TN}$:

→ N is "off", P is active "on"

When V_{IN} is high, i.e. $V_{IN} = V_{DD} - V_{SG} > V_{TP}$:

→ P is "off", N is active "on"


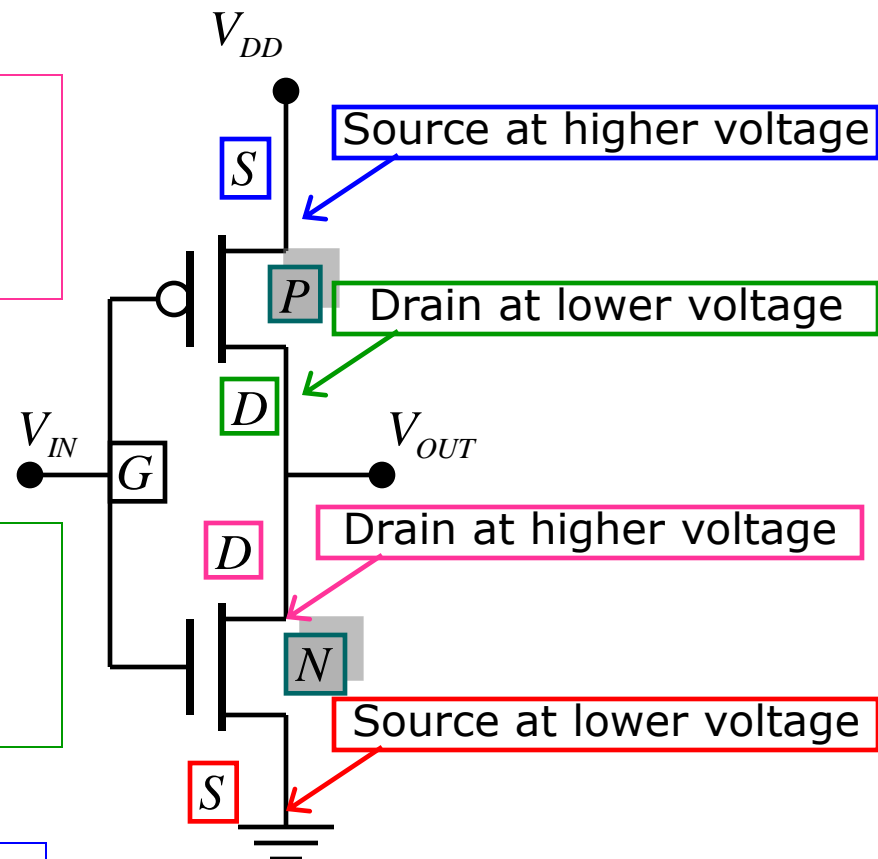
Thus, for input high and low states, both devices never conduct simultaneously



CMOS NAND Gate

V_A	V_B	N_A	N_B	P_A	P_B	V_{OUT}
low	low	off	off	on	on	high
low	high	off	on	on	off	high
high	low	on	off	off	on	high
high	high	on	on	off	off	low



NAND

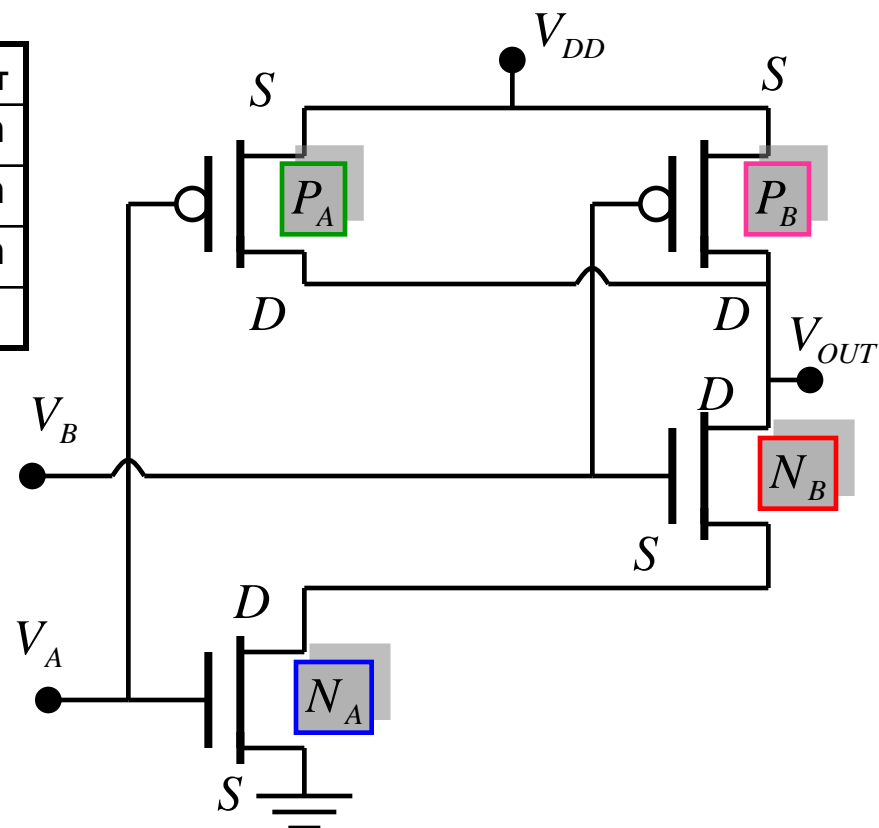 


CMOS NOR Gate

V_A	V_B	N_A	N_B	P_A	P_B	V_{OUT}
low	low	off	off	on	on	high
low	high	off	on	on	off	low
high	low	on	off	off	on	low
high	high	on	on	off	off	low


NOR

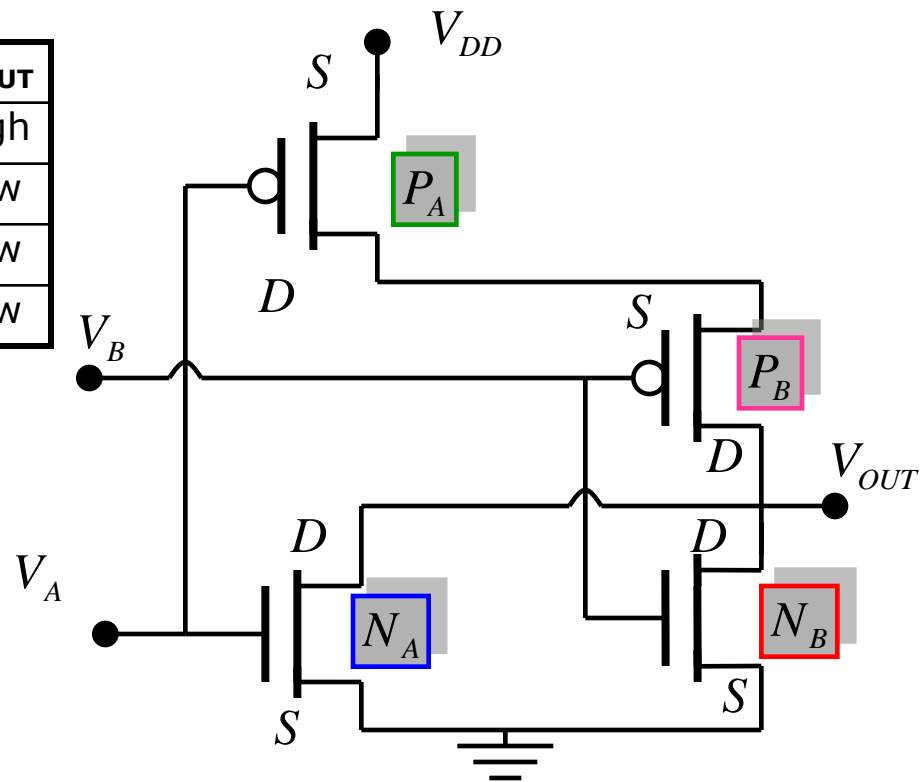 


CMOS AND Gate

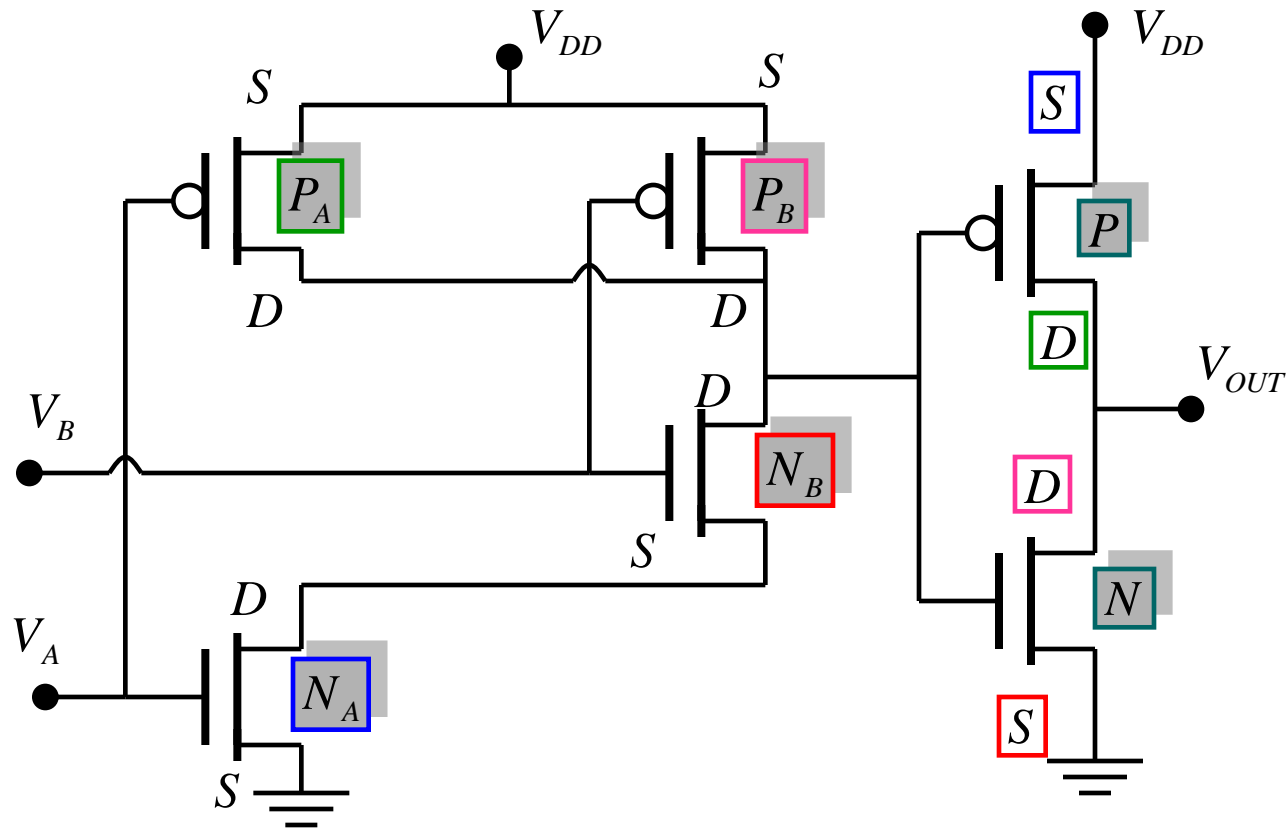


AND

 


CMOS OR Gate

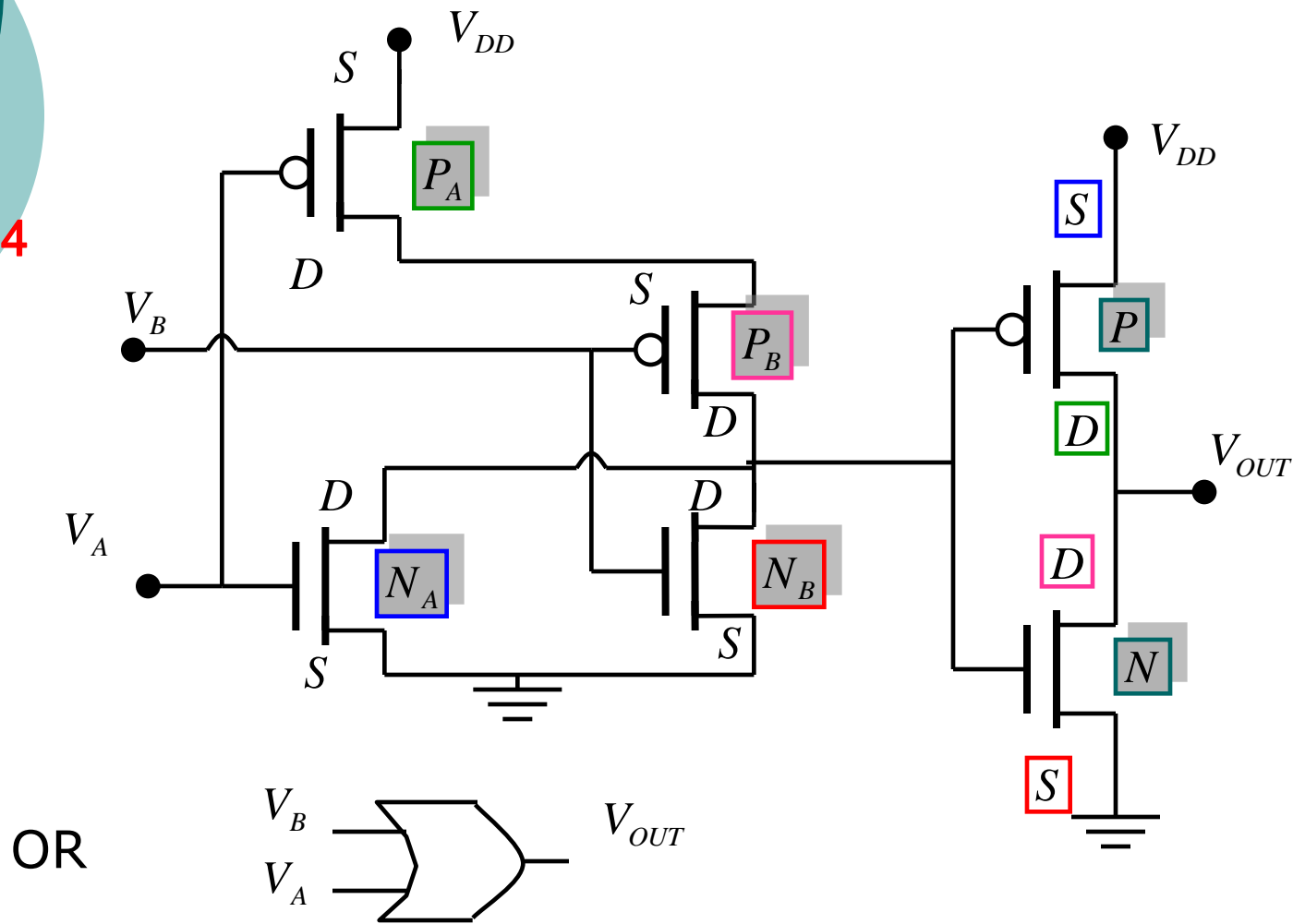

CMOS AND-OR-Inverter Gate

 

CMOS XOR Gate

 

$$F = \overline{A} \cdot A + \overline{A} \cdot B + \overline{B} \cdot A + \overline{B} \cdot B = \overline{A} \cdot B + \overline{B} \cdot A$$

-
- HW #13: Solve Problems: 24.1-6, 24.25