

# CHAPTER SIX

## *Diode- Transistor logic (DTL)*


*Digital Electronics.*

# Introduction

- To improve upon the RTL circuits, DTL circuits are introduced in this chapter.
- The fan-out in RTL gates was relatively low.

# Basic DTL Inverter

© Dr. Anas  
Ch 6

 

For  $\begin{cases} V_I - V_{DI}(ON) + V_{DL}(ON) < V_{BE}(FA) \\ V_I < V_{BE}(FA) \end{cases} \Rightarrow V_X < V_{BE}(FA) + V_{DI}(ON)$


$V_{IL} = V_{BE}(FA)$        $V_{OH} = V_{CC}$        $D_I$  is ON,  
 $D_L$  &  $Q_1$  are OFF

For  $\begin{cases} V_I = V_{BE}(FA) \\ V_X = V_{BE}(FA) + V_{DL}(ON) \end{cases} \Rightarrow D_I \text{ \& } D_L \text{ \& } Q_1 \text{ are ON (FA)}$


For  $\begin{cases} V_I - V_{DI}(ON) + V_{DL}(ON) = V_{BE}(sat) \\ V_I \geq V_{IH} \end{cases} \Rightarrow$

$V_{IH} = V_{BE}(sat)$        $D_I$  is OFF,  
 $D_L$  is ON  
 $Q_1$  is sat

$V_{OL} = V_{CE}(sat)$

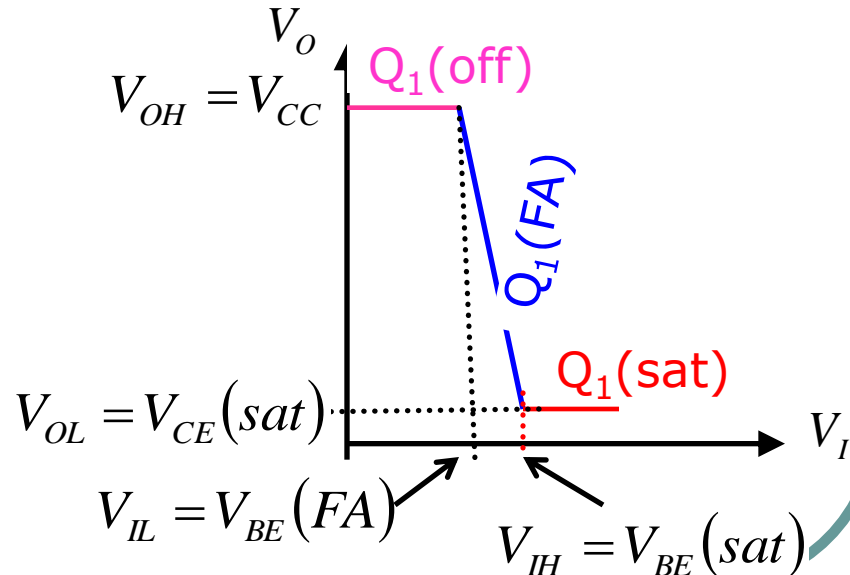

# Basic DTL NAND Gate

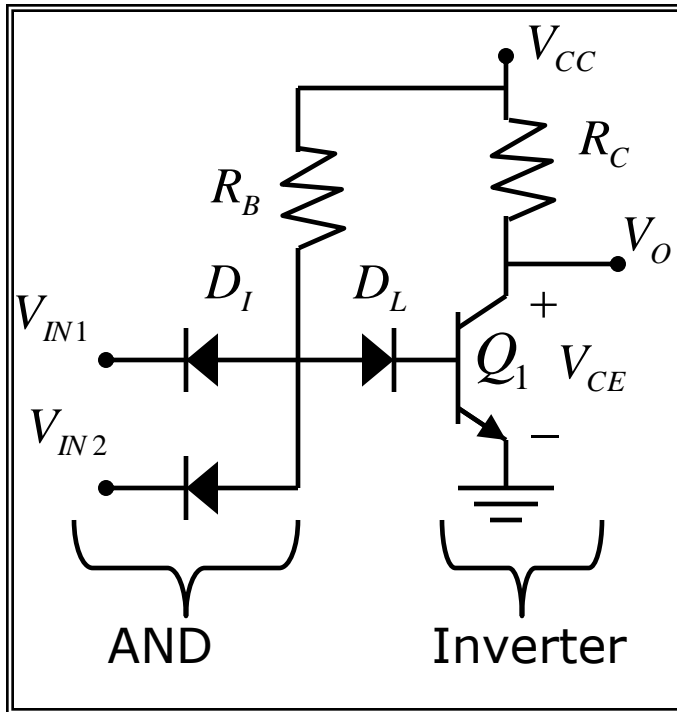

If at least one input less than  $V_{BE}(FA)$ , then  $Q_1$  is off. i.e.  $I_{CC}=0$

$$V_{OH} = V_{CC}$$



# Noise Margins in DTL Gates


- Noise margins:
  - Low noise margin
  - High noise margin

$$V_{NML} = V_{BE}(FA) - V_{CE}(sat)$$

$$V_{NMH} = V_{CC} - V_{BE}(sat)$$

$$V_{NML} = V_{IL} - V_{OL}$$


$$V_{NMH} = V_{OH} - V_{IH}$$

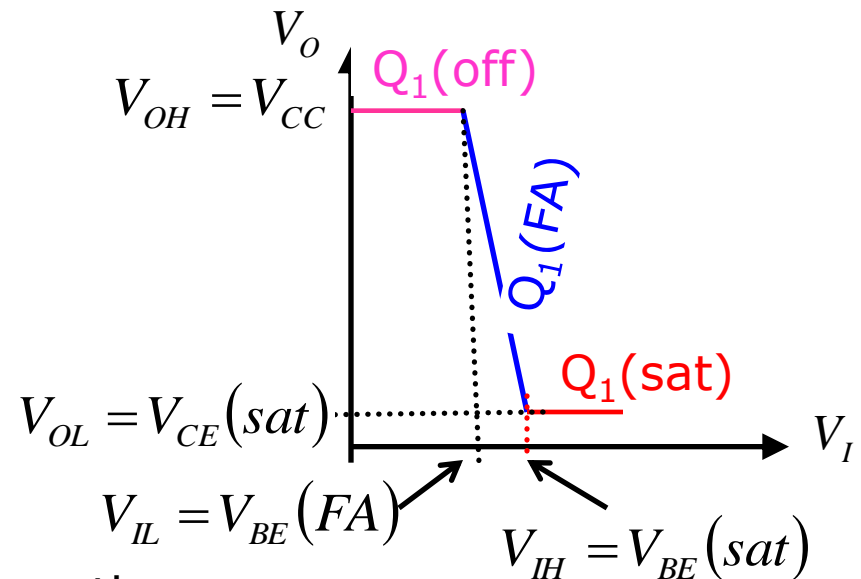

To improve the low noise margin, another diode is connected in series with  $D_L$ .



# Level-Shifted DTL Inverter

 

The **additional diode  $D_{L2}$**  increases both  $V_{IL}$  and  $V_{IH}$  by  $V_{D_{L2}}(ON)$ , i.e. The **VTC** shifts on the x-axis by  $V_{D_{L2}}(ON)$

Low noise margin is improved, while the high noise margin is still accepted.


Ex:  $V_{CE}(sat) = 0.2V$ ,  $V_{BE}(FA) = 0.7V$ ,  
 $V_{BE}(sat) = 0.8V$ ,  $V_{CC} = 5V$ ,

When  $Q_1$  is switched from saturation to cut-off, the stored base charges must be removed in order to make the switching faster. A resistor  $R_D$  &  $V_{EE}(-)$  are added.

Without $D_{L2}$	With $D_{L2}$
$V_{NML} = 0.7 - 0.2$ $= 0.5V$	$V_{NML} = 1.4 - 0.2$ $= 1.2V$
	$\frac{1.2 - 0.5}{0.5} = 140\%$
	$140\% \text{ increase}$
$V_{NMH} = 5 - 0.8$ $= 4.2V$	$V_{NMH} = 5 - 1.5$ $= 3.5V$
	$\frac{3.5 - 4.2}{4.2} = 16.7\%$
	$16.7\% \text{ decrease}$
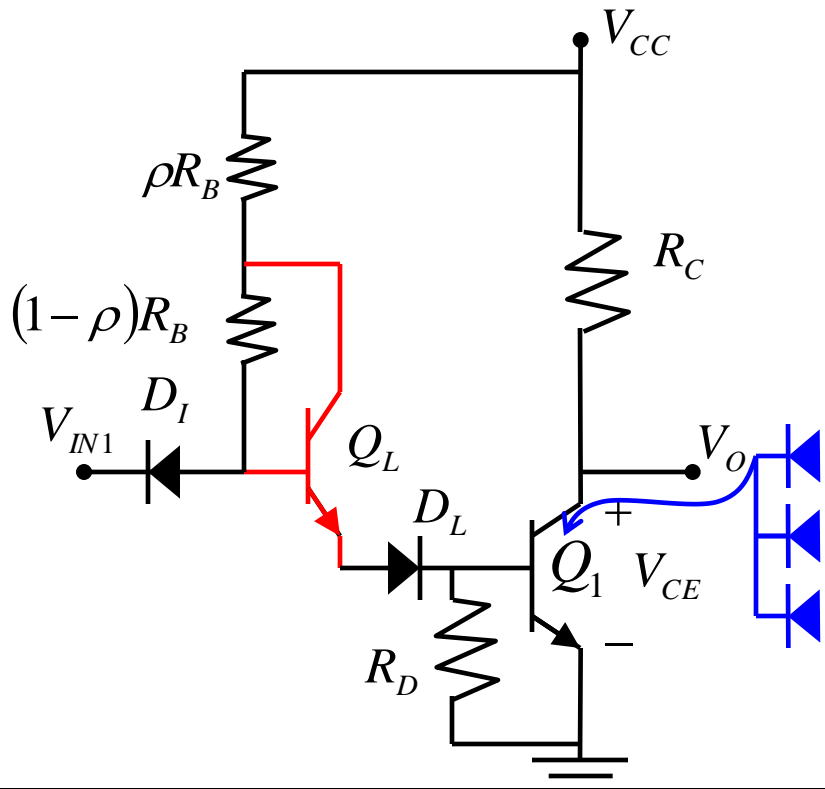
# Transistor Modified DTL

The fan-out can be further improved by replacing the level-shifting diode  $D_{L2}$  with a BJT  $Q_L$ , and splitting  $R_B$  into two resistors  $\rho R_B$  and  $(1-\rho)R_B$ , whose sum is  $R_B$ .




The BJT  $Q_L$ , provides more base current to  $Q_1$ , i.e.  $Q_1$  sinks more current from an output load  $\rightarrow$  fan-out increases.  $Q_L$  operates in forward-active mode ( $V_B < V_C$ ) (emitter-follower configuration).

If  $\rho=1$ ,  $Q_L$  acts as a diode ( $D_{L2}$ )

When splitting  $R_B$ : the input resistance  $R_B$  seen by  $V_{IN}$  (low) remains the same.

When  $V_{IN} > V_{IH}$ :  $Q_L$  is ON (FA)

# Transistor Modified DTL

 

## ● Example

Determine  $V_{OH}$ ,  $V_{OL}$ ,  $V_{IL}$ , and  $V_{IH}$  for TMDTL, assuming  $V_{CE(sat)}=0.2V$ ,  $V_{BE(FA)}=0.7V$ ,  $V_{CC}=5V$ ,  $V_D(ON)=0.7V$

## ● Solution


$$V_{OH} = V_{CC} \quad V_{OL} = V_{CE(sat)}$$

$$V_{IL} = -V_{DI(ON)} + V_{BE,L(FA)} + V_{DL(ON)} + V_{BE,1(FA)}$$

$$V_{IL} = 1.4V$$

$$V_{IH} = -V_{DI(ON)} + V_{BE,L(FA)} + V_{DL(ON)} + V_{BE,1(sat)}$$

$$V_{IH} = 1.5V$$

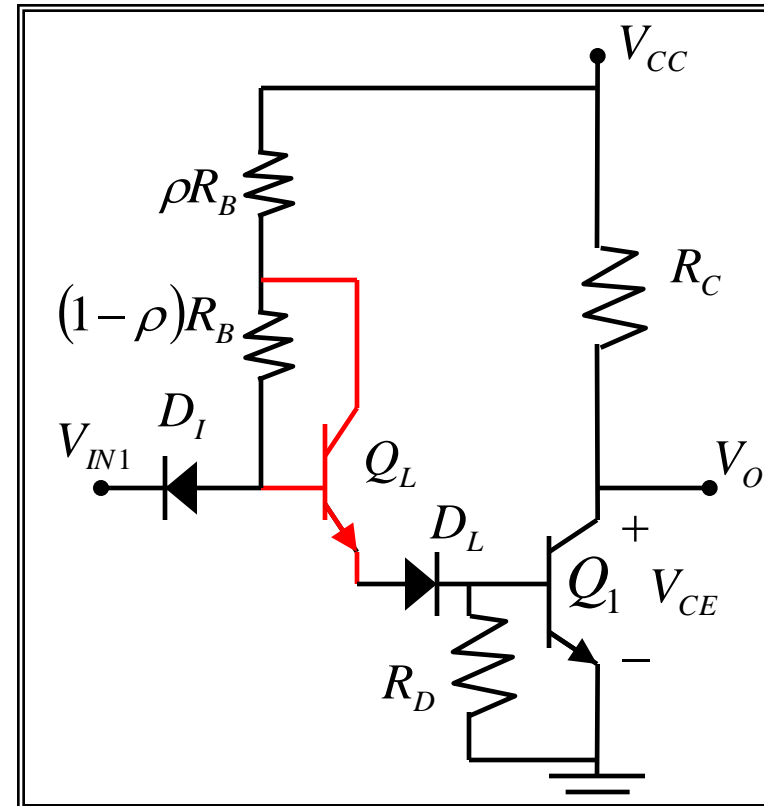




# DTL NAND Gate

The VTC is similar to the basic DTL NAND gate, (refer to slide 5)

When any input is low, then  $Q_L$ ,  $Q_1$  are off. Therefore,  $V_{OH} = V_{CC}$ .

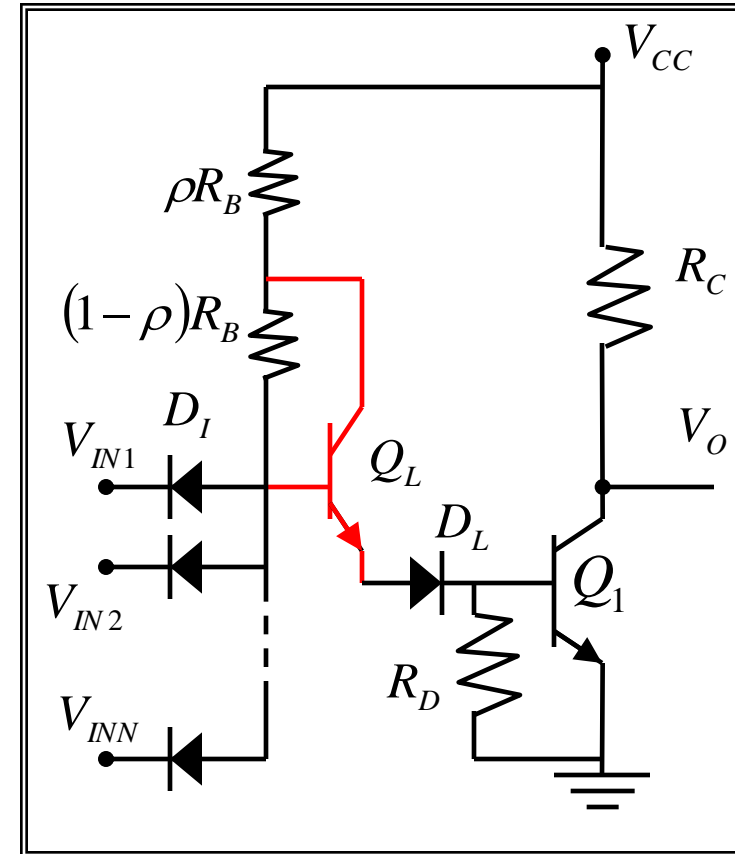When all input are high, then  $Q_L$  (FA),  $Q_1$  (sat) are ON. Therefore,  $V_{OL} = V_{CE}(\text{sat})$ .



# DTL Fan-Out

When the output voltage is at state high, then the input diodes in the load gates are reverse-biased


When the output voltage is at state low, then the input diodes in the load gates are forward-biased

Maximum fan-out depends on the last statement

$$I_{OL} = M \times I_{IL}$$




$$M = \frac{I_{OL}}{I_{IL}}$$

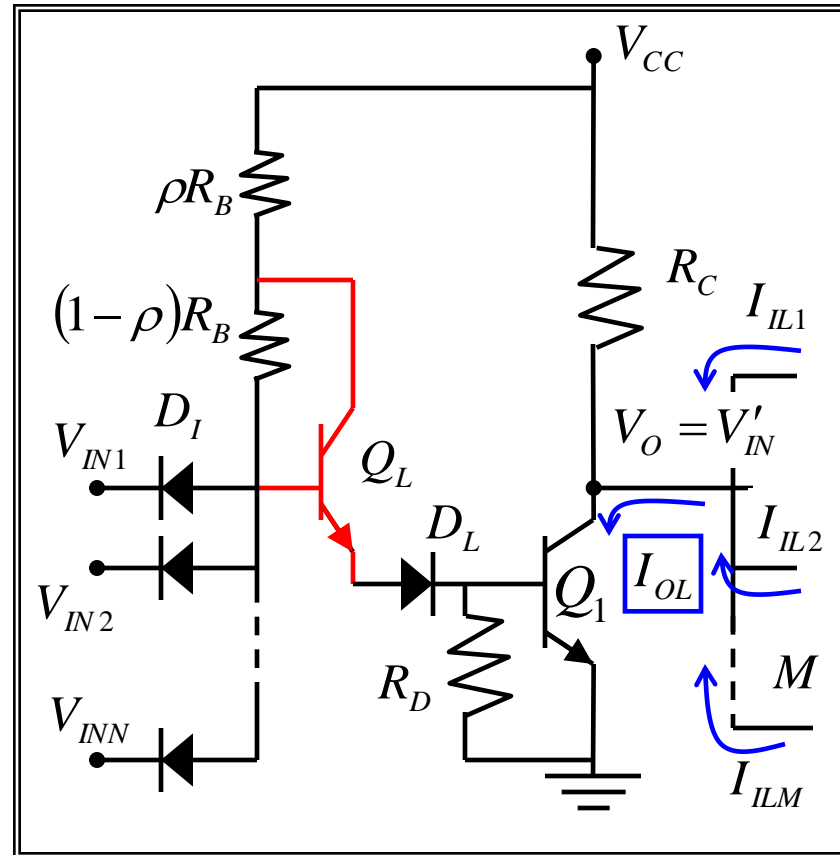
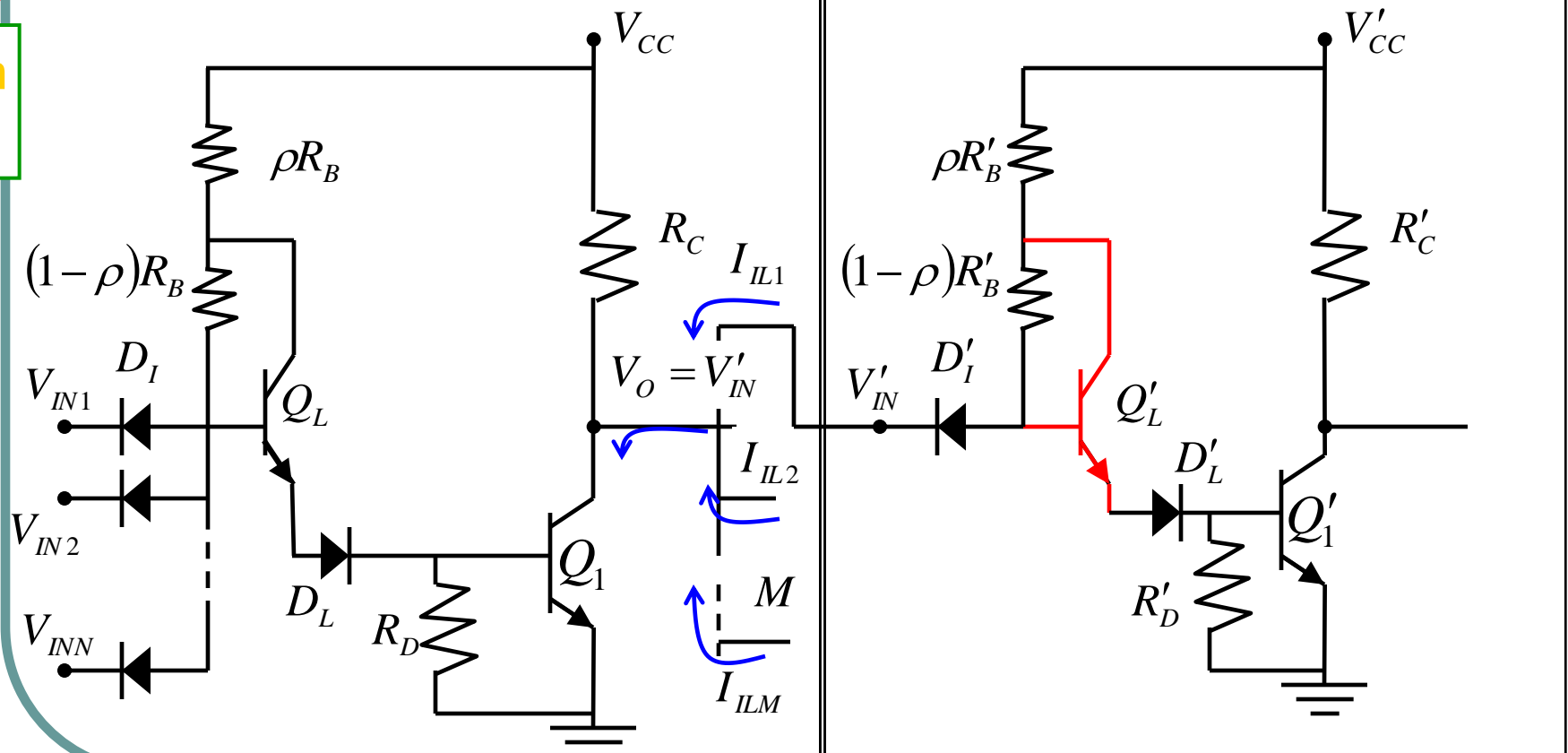
# DTL Fan-Out

Input current low  $I_{IL}$


$$I_{IL} = \frac{V'_{CC} - V'_D(ON) - V_{CE}(sat)}{R'_B}$$


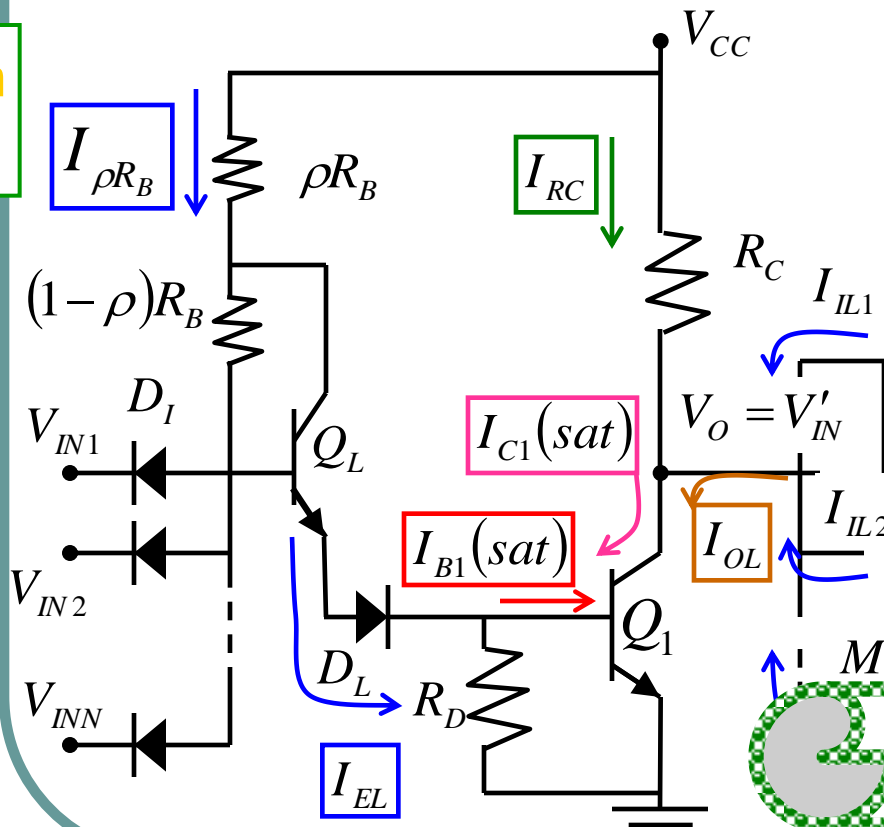
# DTL Fan-Out

Input current low  $I_{IL}$

$$I_{IL} = \frac{V'_{CC} - V'_D(ON) - V_{CE}(sat)}{R'_B}$$



Output current low  $I_{OL}$

$$I_{OL} = I_{C1}(sat) - I_{RC}$$

$$I_{OL} = \sigma_1 \beta_F I_{B1}(sat) - \frac{V_{CC} - V_{CE}(sat)}{R_C}$$


$$I_{B1}(sat) = I_{EL} - \frac{V_{BE}(sat)}{R_D}$$

$$I_{EL} = I_{\rho R_B}$$

Assuming  $I_{BL}$  negligible, we can neglect the voltage drop across  $(1-\rho)R_B$ .

$$I_{\rho R_B} \cong \frac{V_{CC} - V_{BE,L}(FA) - V_D(ON) - V_{BE1}(sat)}{\rho R_B}$$

# DTL Fan-Out

 

## ● Example

Determine the maximum **fan-out** for driving DTL gate, assuming:

$$V_{CE}(sat)=0.2V, V_{BE}(sat)=0.8V,$$

$$V_{BE}(FA)=0.7V, V_D(ON)=0.7V, V_{CC}=5V,$$


$$R_C=6k\Omega, \rho R_B=1.75k\Omega, (1-\rho)R_B=2k\Omega, R_D=5k\Omega,$$

$$\beta_F=49, \text{ and } \sigma_{1L}=0.85.$$

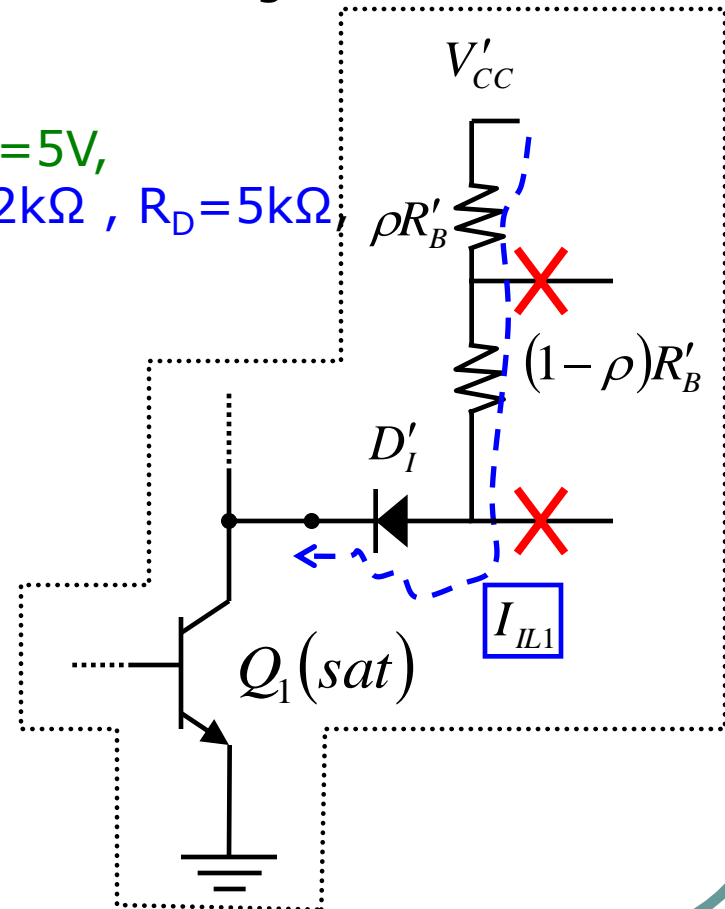
## ● Solution

$$I_{IL} = \frac{V'_{CC} - V'_D(ON) - V_{CE}(sat)}{R'_B}$$

$$I_{IL} = \frac{5 - 0.7 - 0.2}{3.75} = 1.093mA$$



# DTL Fan-Out

 

## ● Example

Determine the maximum **fan-out** for driving DTL gate, assuming:

$$V_{CE}(sat)=0.2V, V_{BE}(sat)=0.8V,$$

$$V_{BE}(FA)=0.7V, V_D(ON)=0.7V, V_{CC}=5V,$$

$$R_C=6k\Omega, \rho R_B=1.75k\Omega, (1-\rho)R_B=2k\Omega, R_D=5k\Omega,$$

$$\beta_F=49, \text{ and } \sigma_{1L}=0.85.$$

## ● Solution

$$I_{IL} = 1.093mA$$


$$I_{\rho R_B} \cong \frac{V_{CC} - V_{BE,L}(FA) - V_D(ON) - V_{BE1}(sat)}{\rho R_B}$$

$$I_{\rho R_B} \cong \frac{5 - 0.7 - 0.7 - 0.8}{1.75} = 1.6mA = I_{EL}$$

$$I_{B1}(sat) = I_{EL} - \frac{V_{BE}(sat)}{R_D} = 1.6 - \frac{0.8}{5} = 1.44mA$$

$$I_{OL} = 0.85 \times 49 \times 1.44 - \frac{5 - 0.2}{6} = 59.98 - 0.8 = 59.18mA$$
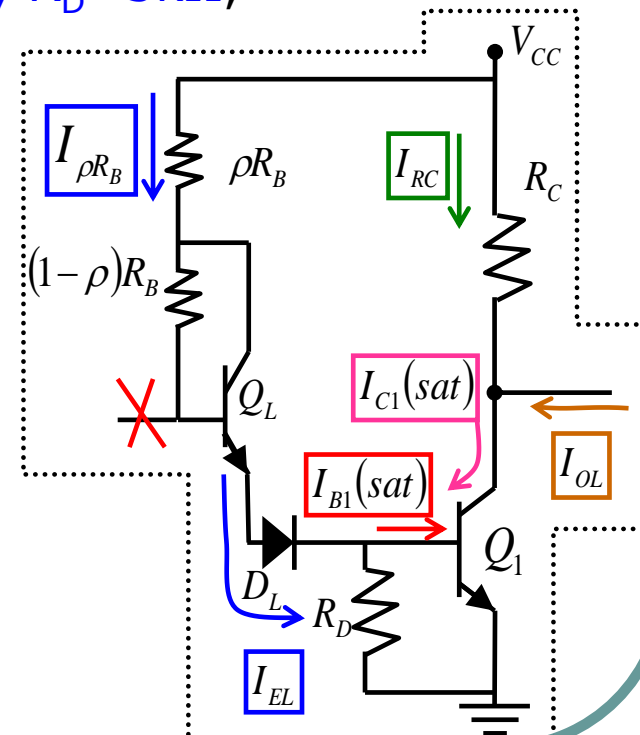
$$M = \frac{I_{OL}}{I_{IL}} = \frac{59.18}{1.093} = 54.4 \quad \boxed{M = 54}$$



# DTL Power-Dissipation

Output high current supplied ( $I_{CC}(H)$ )  
For High output, Input is low ( $V_{CE}(sat)$ )

$$I_{\rho R_B}(H) \cong \frac{V_{CC} - V_D(ON) - V_{CE1}(sat)}{R_B}$$

Since  $Q_1$  is cut-off,  $I_{RC}(OH) = 0 \rightarrow I_{CC(Total)}(OH) = I_{\rho RB}(OH)$

Output low current supplied ( $I_{CC}(L)$ )  
For Low output, Input is High

$$I_{\rho R_B}(L) \cong \frac{V_{CC} - V_{BE,L}(FA) - V_D(ON) - V_{BE1}(sat)}{\rho R_B}$$

$$I_{RC}(L) = \frac{V_{CC} - V_{CE}(sat)}{R_C}$$

$$I_{CC}(L) = I_{RC}(L) + I_{\rho RB}(L)$$

- HW #6: Solve Problems: 6.1 , 6.5, 6.8, 6.12, 6.14