


 
CHAPTER SEVEN

Transistor- Transistor logic (TTL)

Digital Electronics.

Introduction

Diode-**T**ransistor **L**ogic  **T**ransistor-**T**ransistor **L**ogic




The TTL circuits provide

1. Increased fan-out.
2. Improved transient response.
3. Reduction in chip area.
4. Inclusion of an active pull-up circuits


Basic TTL Inverter

© Dr. Anas
Ch 7

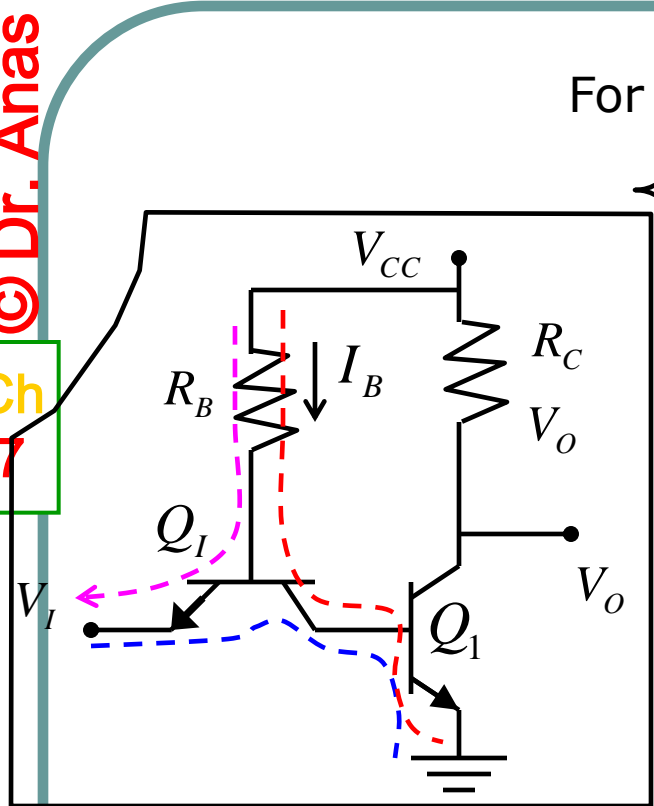

For $V_I \leq V_{IL} = V_{BE,1}(FA) - V_{CE,I}(sat) \Rightarrow$ BE of Q_I is forward-biased
 $I_B = \frac{V_{CC} - V_{BE,I} - V_I}{R_B}$ For typical values of R_B , I_B is in mA, Q_I is sat.
 $V_{BE,1} = V_{CE,I}(sat) + V_{IL}$ Q_1 is cut-off $V_{OH} = V_{CC}$


 
For $V_I \geq V_{IL} \Rightarrow Q_I$ is sat & Q_1 is FA



For $V_I = V_{IH} = V_{BE,1}(sat) - V_{CE,I}(sat)$
 $V_{OL} = V_{CE}(sat) \Rightarrow Q_1$ is sat

3 For $V_I > V_{IH}$ BE of Q_I is reverse-biased
 Inverse-active mode (RB)


Basic TTL Inverter

  


- The input and level-shifting diodes are replaced by Q_I
- The Q_I BJT requires less area than the two diodes

Stored-Charge Removal in TTL

cct's

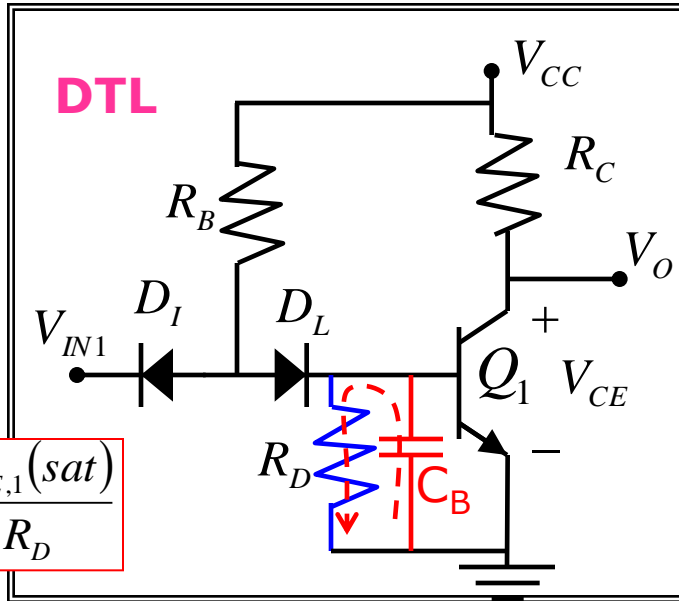

$$I_{SCR} = \frac{V_{BE,1}(sat)}{R_D}$$

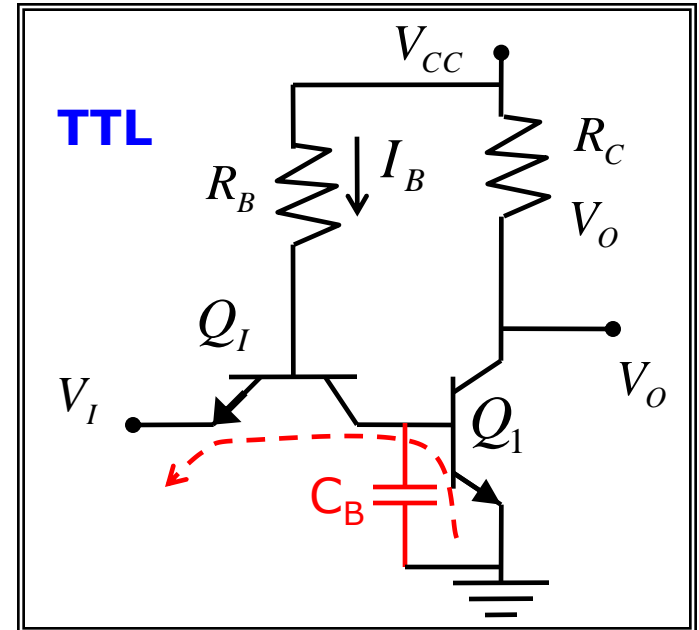

When V_I changes from High (V_{IH}) to Low (V_{IL}), Q_1 is switched from saturation to cut-off, the stored base charges in C_B must be removed.


$V_{C,I} = V_{C_B} = V_{BE,1}(sat)$ $V_{BC,I} = V_{B,I} - V_{C,I} = V_{BE,1}(FA) + V_{IL} - V_{BE,1}(sat)$ $V_{BC,I} \cong 0.1V$
 BC junction of Q_1 is slightly forward-biased but insufficient to saturate $Q_1 \rightarrow Q_1$ is **F.A.**

$$I_{C,I} = \beta_F \left(\frac{V_{CC} - V_{BE,1}(FA) - V_{CE,1}(sat)}{R_B} \right)$$

Discharge current $I_{C,I}$

Stored-Charge Removal in TTL

cct's

 

● Example

Calculate the improvement factor in stored charge removal for TTL over DTL circuits assuming:

$V_{CE(sat)}=0.2V$, $V_{BE(FA)}=0.7V$, $V_{BE(sat)}=0.8V$,
 $V_{CC}=5V$, $R_B=2k\Omega$, $R_D=5k\Omega$, and $\beta_F=50$.


● Solution

$$\text{In DTL } I_{SCR} = \frac{V_{BE,1}(sat)}{R_D} = \frac{0.8}{5} = 0.16mA$$

$$\text{In TTL } I_{C,I} = \beta_F \left(\frac{V_{CC} - V_{BE,I}(FA) - V_{CE,1}(sat)}{R_B} \right) = 50 \left(\frac{5 - 0.7 - 0.2}{2} \right)$$

$$I_{C,I} = 102.5mA$$

$$\text{Improvement factor} = 640.6$$

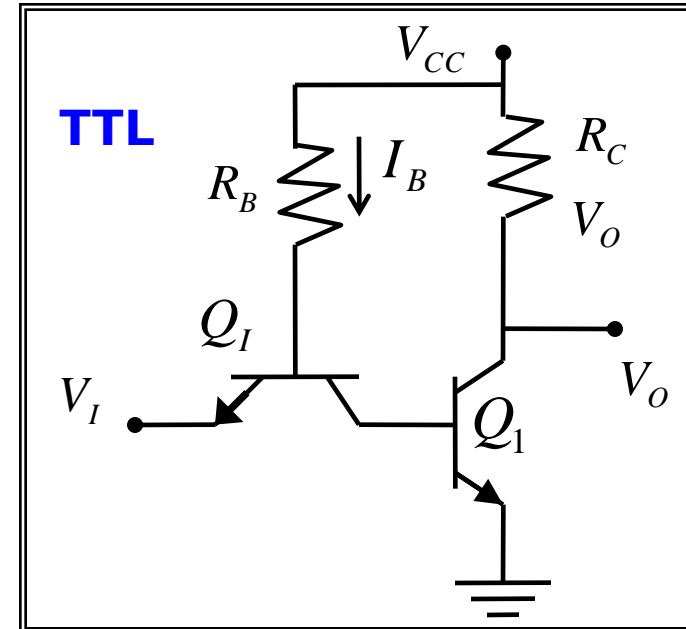


Basic TTL NAND Gate

If at least one input is less than V_{IL} , then the Q_1 is off.

$$V_{OH} = V_{CC}$$


If all inputs are greater than V_{IH} , then the Q_1 is sat.

$$V_O = V_{CE}(sat)$$

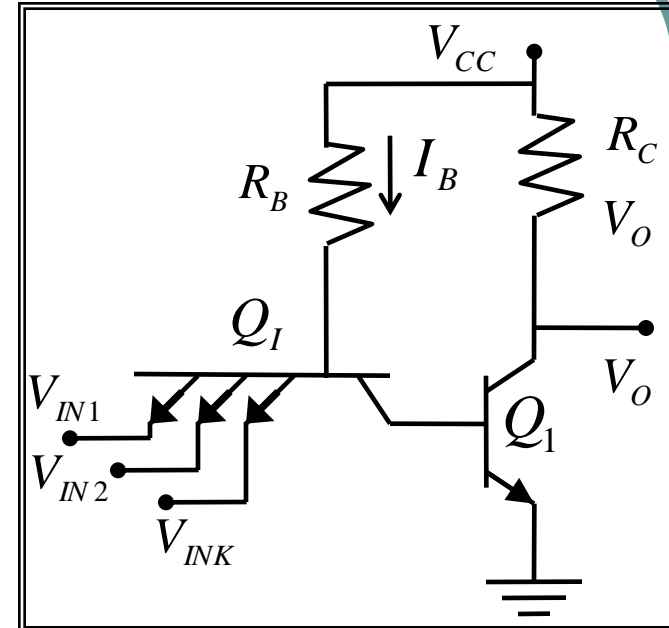

Multiple-emitter BJT requires much less chip area than using individual transistors for each input

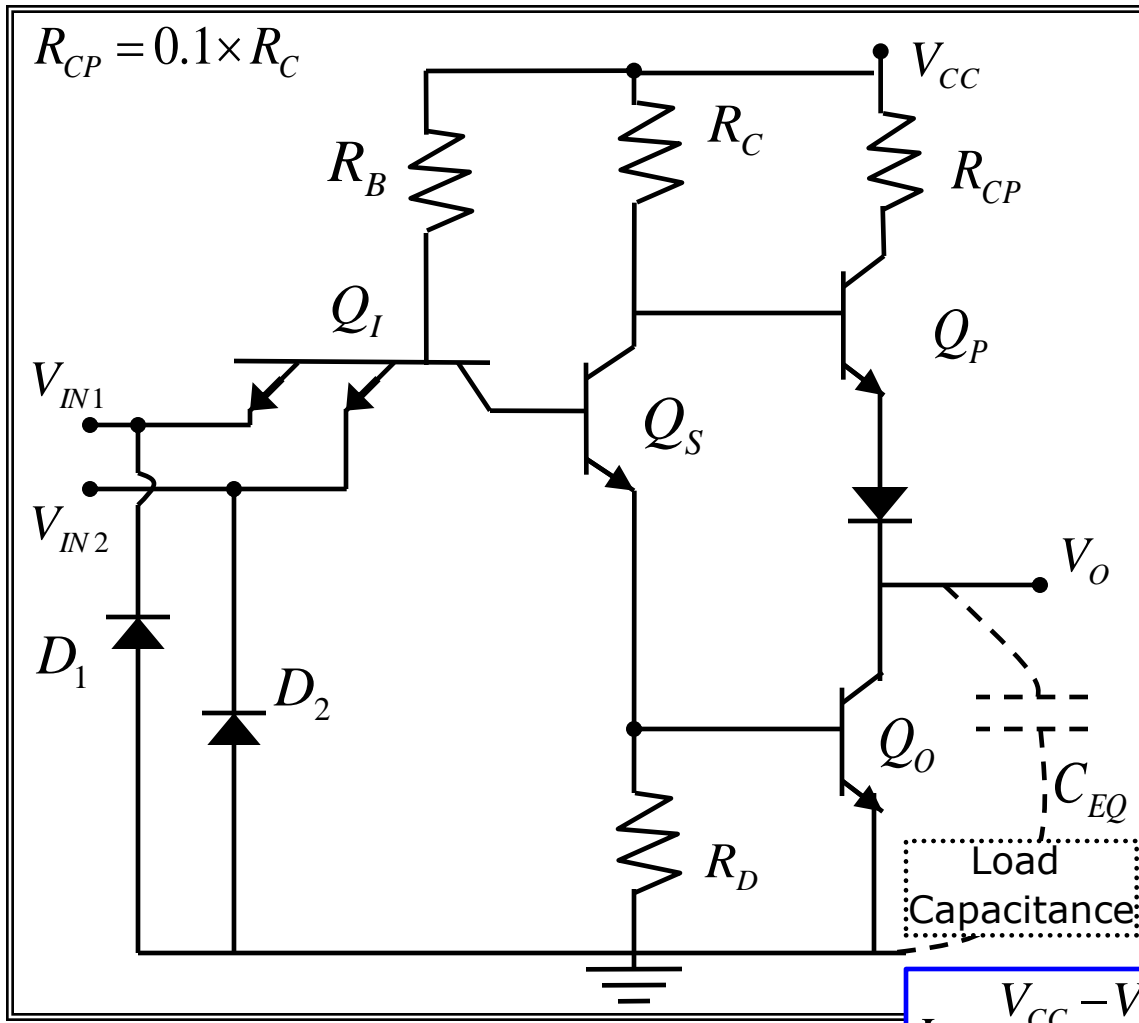Standard TTL NAND Gate With Totem Pole Output



In **basic** TTL: C_{EQ} is charged through R_C

$$\tau = R_C \times C_{EQ}$$

Initial charge current

$$I_i = \frac{V_{CC} - V_{CE}(sat)}{R_C}$$

In **standard** TTL: C_{EQ} is charged through R_{CP}


$$\tau = R_{CP} \times C_{EQ}$$

Initial charge current

$$I_i = \frac{V_{CC} - V_D(ON) - V_{CE,P}(sat) - V_{CE,O}(sat)}{R_{CP}}$$

Since $R_{CP} \ll R_C$, standard TTL has much smaller rise time

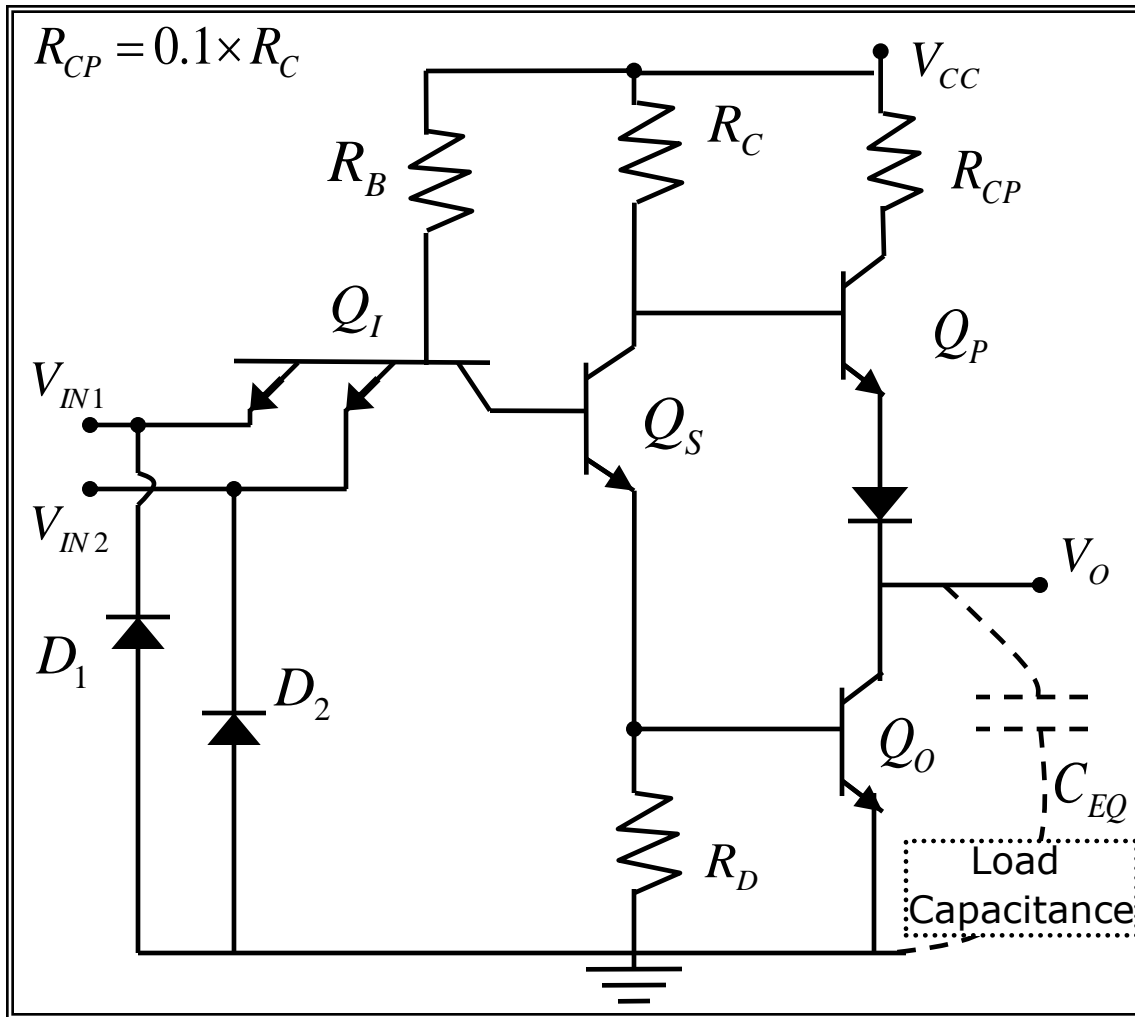Standard TTL NAND Gate With Totem Pole Output




Function of R_D :

In basic TTL, the stored charge of Q_O is removed by Q_I .

In STTL, Q_I no longer sinks the base current of Q_O . Therefore, this removal is done by R_D since Q_O is not heavily sat.

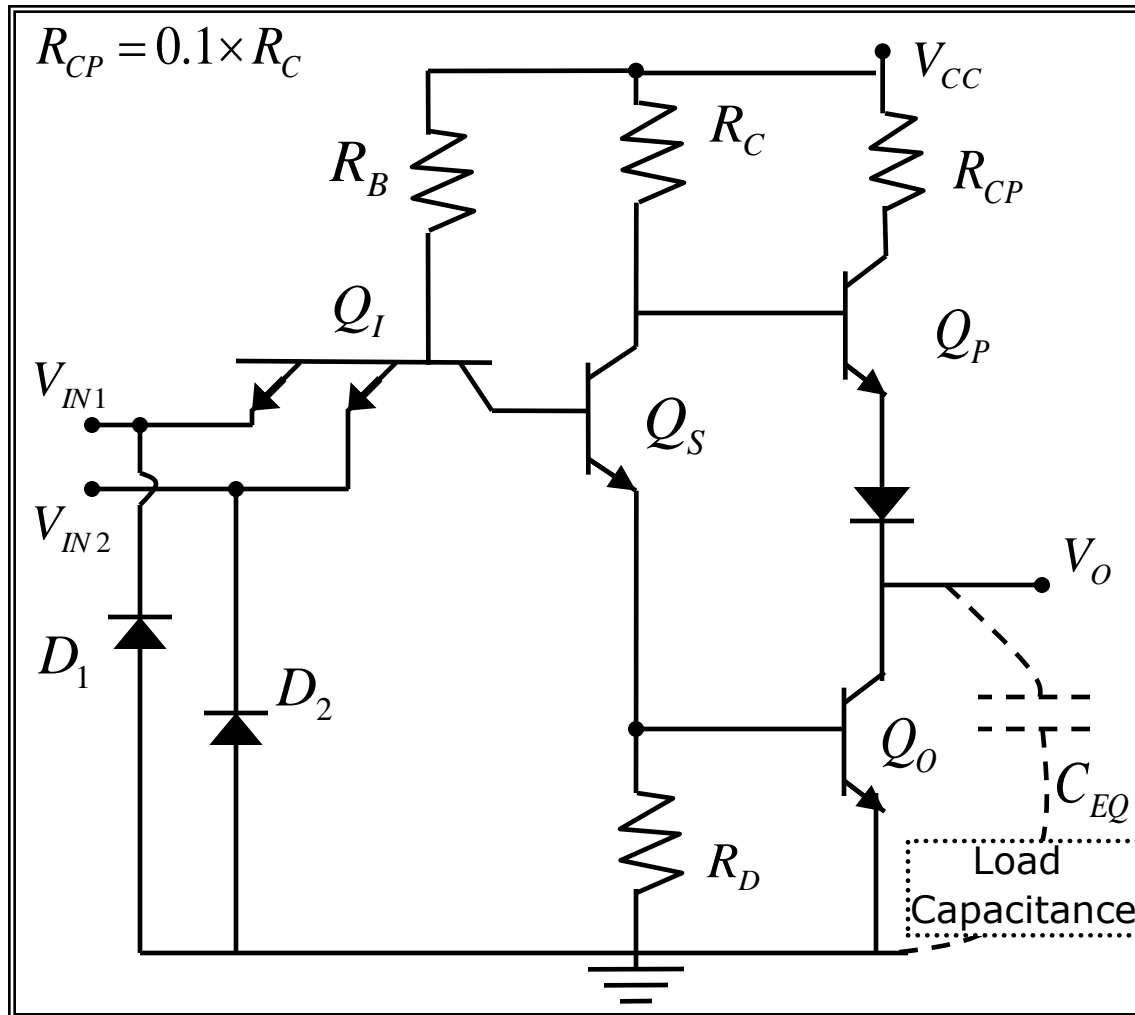Standard TTL NAND Gate With Totem Pole Output



Function of D_1 & D_2 :

The clamping diodes are used to limit the negative swing of the input voltages to one diode drop below ground

Standard TTL VTC

$$\frac{V_{OH}}$$

When V_{IN} is low:

$$I_{B,I} = \left(\frac{V_{CC} - V_{BE,I}(sat) - V_{IL}}{R_B} \right)$$

The collector current I_{CI} of Q_I is

$$I_{C,I} = -I_{B,S(SCR)} \ll \beta_F I_{B,I}$$


Therefore, Q_I is sat.

$$V_{B,S} = V_{IL} + V_{CE,I}(sat) < V_{BE,S}(FA)$$

Q_S and Q_O are off.

$$V_{OH} = V_{CC} - V_{BE,P}(FA) - V_D(ON)$$

(Neglecting I_{BP} .)

 

$$I_{BP,I} = \frac{V_{CC} - V_{BE,P}(FA) - V_D(ON)}{R_C + (1 + \beta_F) \times R_{MI}}$$

$\approx 10M\Omega$

Standard TTL VTC

V_{IL}

As V_I increases to :

$$V_I = -V_{CE,I}(sat) + V_{BE,S}(FA)$$

Q_S starts conducting

$$V_{IL} = V_{BE,S}(FA) - V_{CE,I}(sat)$$

→ Q_I & Q_S are ON, Q_O is OFF

As V_I increases further to :

$$V_I = -V_{CE,I}(sat) + V_{BE,S}(FA) + V_{BE,O}(FA)$$

Q_O becomes FA


$$V_{IB} = 2V_{BE}(FA) - V_{CE,I}(sat)$$

V_{IB} is called Input Breakpoint Voltage



V_{OB} is the output voltage that corresponds V_{IB} can be found just as Q_O turns ON.
 
$$I_{RC} = I_{RD} = \frac{V_{BE,O}(FA)}{R_D} \Rightarrow V_{OB} = V_{CC} - R_C I_{RC} - V_{BE,P}(FA) - V_D(ON)$$



Standard TTL VTC

$$\frac{V_{IH}}$$


Q_O and Q_S are sat when

$$V_I = -V_{CE,I}(sat) + V_{BE,S}(sat) + V_{BE,O}(sat)$$


$$V_{IH} = 2V_{BE}(sat) - V_{CE,I}(sat)$$

$$V_{IL} = V_{BE,S}(FA) - V_{CE,I}(sat)$$

$$V_{OL} = V_{CE,O}(sat)$$

 

Standard TTL VTC

 

Example

Plot the VTC of standard TTL circuits assuming:

$V_{CE}(\text{sat})=0.2\text{V}$, $V_{BE}(\text{FA})=0.7\text{V}$,
 $V_{BE}(\text{sat})=0.8\text{V}$, $V_{CC}=5\text{V}$,
 $R_B=4\text{k}\Omega$, $R_C=1.6\text{k}\Omega$, $R_{CP}=100\Omega$,
 $R_D=1\text{k}\Omega$, and $\beta_F=100$.

Solution



$$V_{OH} = 5 - 1.4 = 3.6\text{V}$$

$$V_{IL} = -0.2 + 0.7 = 0.5\text{V}$$


$$V_{IB} = -0.2 + 1.4 = 1.2\text{V}$$

$$\begin{aligned}
 V_{OB} &= 5 - \frac{0.7}{1} \times 1.6 - 1.4 \\
 &= 2.48\text{V}
 \end{aligned}$$

$$V_{OL} = 0.2\text{V}$$

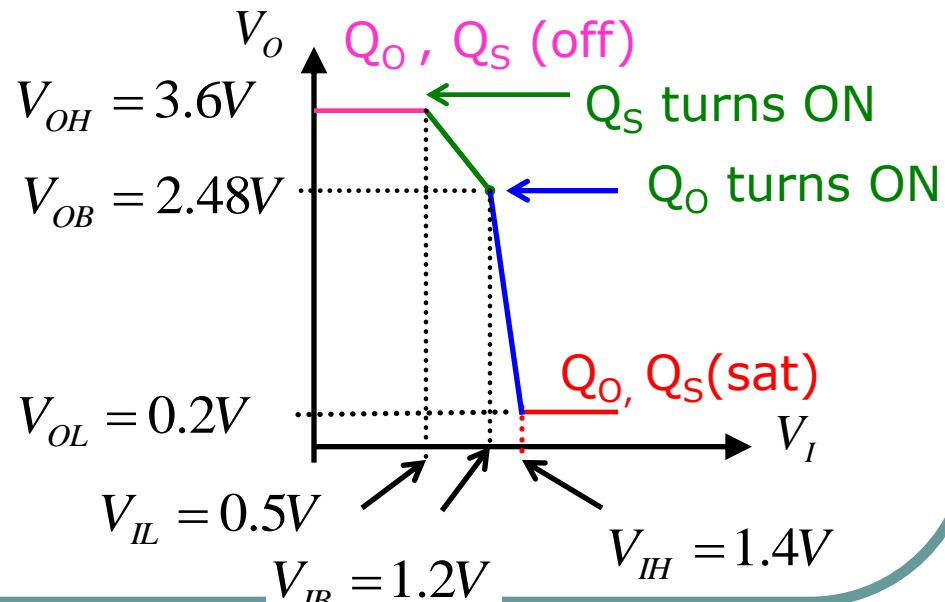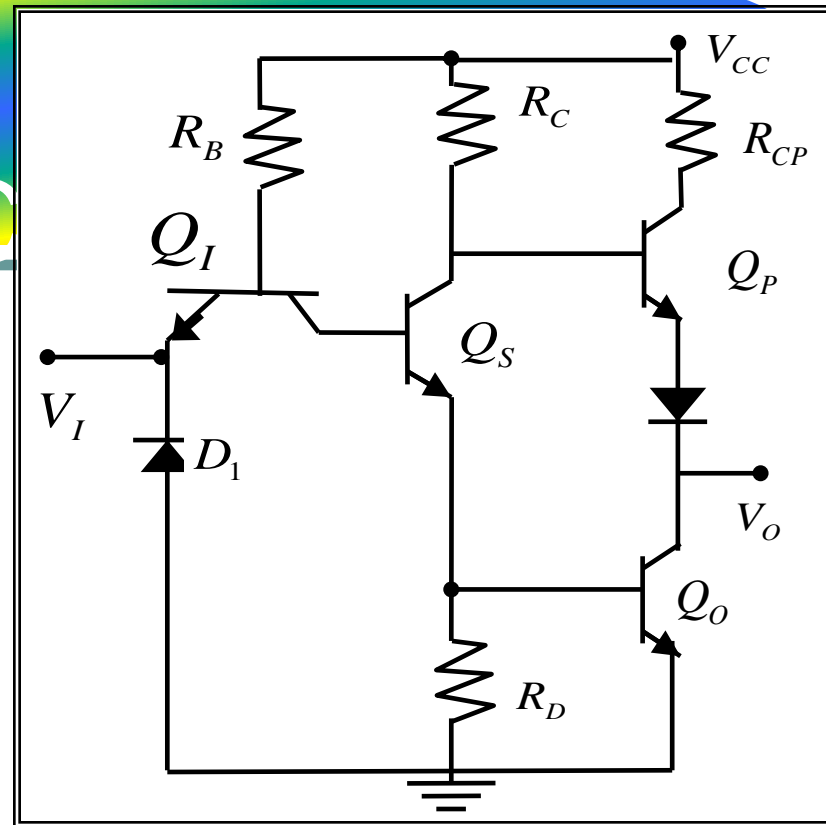


TTL SPICE Simulation

 

● Example

 - *Repeat the last example using PSPICE
- *Plot V_O as a function of V_I
- *Refer to pages 93-94 in the text book.



TTL Fan-Out

When the output is high, I_{IL} is negligible.
Therefore, Fan-out depends on the output low state


$$M = \frac{I_{OL}}{I_{IL}}$$

Input current low I_{IL}

For the input low state, Q_I is sat and Q_S is cut-off

$$I_{CI} = -I_{BS} (\cong 0)$$
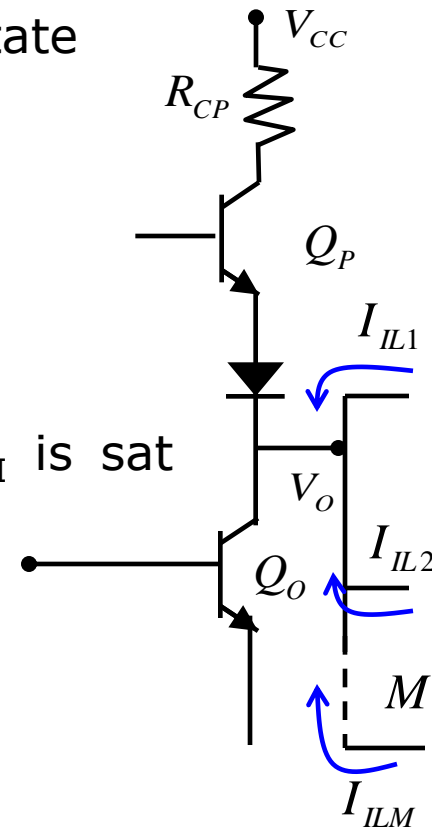
$$I_{IL} = I_{EI} = I_{RB} = \frac{V'_{CC} - V'_{BE}(sat) - V_{CE,O}(sat)}{R'_B}$$



TTL Fan-Out

I_{IL1}

Output current low I_{OL}

$I_{OL} = I_{C,O}(sat)$ Since the output Q_P and D_L are cut-off

$$I_{OL} = \sigma_{OL} \beta_F I_{BO}(sat)$$


$$I_{BO} = I_{ES}(sat) - \frac{V_{BE,O}(sat)}{R_D}$$

$$I_{ES}(sat) = I_{CS}(sat) + I_{BS}(sat)$$


$$I_{CS}(sat) = \frac{V_{CC} - V_{CE,S}(sat) - V_{BE,O}(sat)}{R_C}$$

$$I_{CI}(RA) = I_{BS}(sat) = I_{BI}(RA) + K \times I_{EI}(RA) = I_{BI}(RA) + \beta_R \times K \times I_{BI}(RA)$$
 
$$I_{BS}(sat) = (1 + K \times \beta_R) \times I_{BI} = (1 + K \times \beta_R) \times \left(\frac{V_{CC} - V_{BC,I}(RA) - V_{BE,S}(sat) - V_{BE,O}(sat)}{R_B} \right)$$



TTL Fan-Out

 

● Example

Calculate the maximum fan-out of TTL circuits assuming:

$V_{CE}(\text{sat})=0.2\text{V}$, $V_{BE}(\text{FA})=0.7\text{V}$, $V_{BE}(\text{sat})=0.8\text{V}$,
 $V_{CC}=5\text{V}$, $R_B=4\text{k}\Omega$, $R_C=1.6\text{k}\Omega$, $R_{CP}=120\Omega$,
 $R_D=1\text{k}\Omega$, $\beta_F=25$, $\beta_R=0.1$, and $\sigma_{OL}=0.85$

● Solution

$$I_{IL} = \frac{5 - 0.8 - 0.2}{4} = 1\text{mA}$$

$$\|M = 51\|$$

$$I_{BS}(\text{sat}) = (1 + 1 \times 0.1) \times \left(\frac{5 - 0.7 - 1.6}{4} \right) = 0.743\text{mA}$$

$$I_{CS}(\text{sat}) = \frac{5 - 0.2 - 0.8}{1.6} = 2.5\text{mA}$$

$$I_{IS}(\text{sat}) = 0.743 + 2.5 = 3.243\text{mA}$$

$$I_{BO} = 3.243 - \frac{0.8}{1} = 2.443\text{mA}$$

$$I_{OL} = 0.85 \times 25 \times 2.443 = 51.9$$




TTL Power-Dissipation

Output high current supplied ($I_{CC}(H)$)
For High output, Input is low ($V_{CE}(sat)$)

$$I_{CC}(OH) = I_{RB} = \frac{V_{CC} - V_{BE}(sat) - V_{CE,O}(sat)}{R_B}$$

 Since Q_S is cut-off, and I_{BP} is very small




TTL Power-Dissipation

Output low current supplied ($I_{CC}(L)$)
For Low output, Input is High


$$I_{CC}(OL) = I_{RC}(sat) + I_{RB}(RA)$$

$$I_{RC}(sat) = \frac{V_{CC} - V_{CE,S}(sat) - V_{BE,0}(sat)}{R_C}$$
 
$$I_{RB}(RA) = \frac{V_{CC} - V_{BC,I}(RA) - 2V_{BE}(sat)}{R_B}$$



TTL Power-Dissipation

 

- **Example**

Calculate the average dissipated power of standard TTL circuits assuming:

$V_{CE}(\text{sat})=0.2\text{V}$, $V_{BE}(\text{FA})=0.7\text{V}$,
 $V_{BE}(\text{sat})=0.8\text{V}$, $V_{CC}=5\text{V}$,
 $R_B=4\text{k}\Omega$, $R_C=1.6\text{k}\Omega$, $R_{CP}=100\Omega$,
 $R_D=1\text{k}\Omega$, and $\beta_F=100$.


- **Solution**

$$I_{CC}(\text{OH}) = I_{RB} = \frac{5 - 0.8 - 0.2}{4} = 1\text{mA}$$


$$I_{CC}(\text{OL}) = \frac{5 - 0.2 - 0.8}{1.6} + \frac{5 - 0.7 - 1.6}{4} \\ = 2.5 + 0.675 = 3.175\text{mA}$$

$$P_{CC}(\text{avg}) = 0.5 \times 4.175 \times 5 = 10.44\text{mW}$$

Low Power TTL (LTTL)

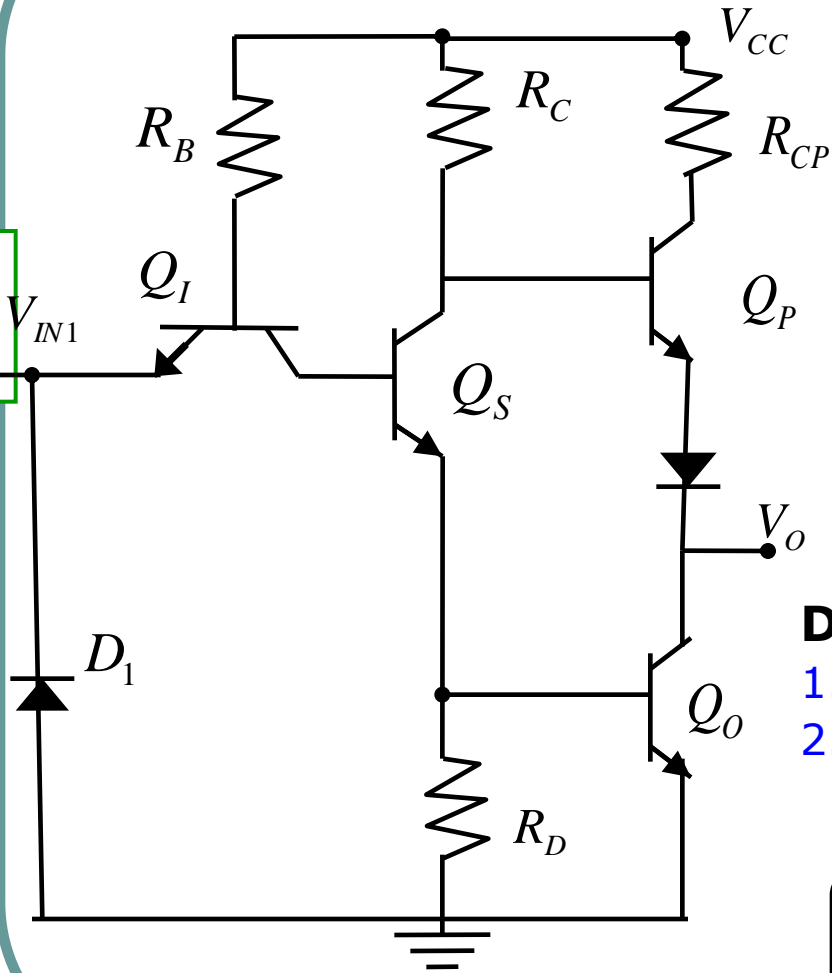

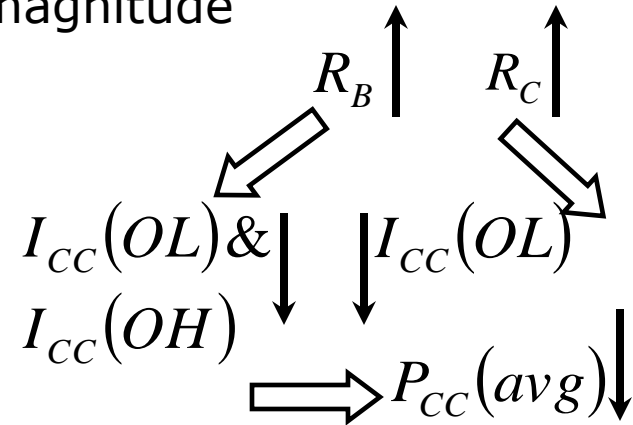This is achieved by increasing resistor values by one order of magnitude





Disadvantages:

1. Fan-Out decreases (refer to slides 16 & 17)
2. Switching speed decreases (transient response gets longer)

Trade off exists between power dissipation and transient response

Low Power TTL (LTTL)


© Dr. Anas
Ch 7

 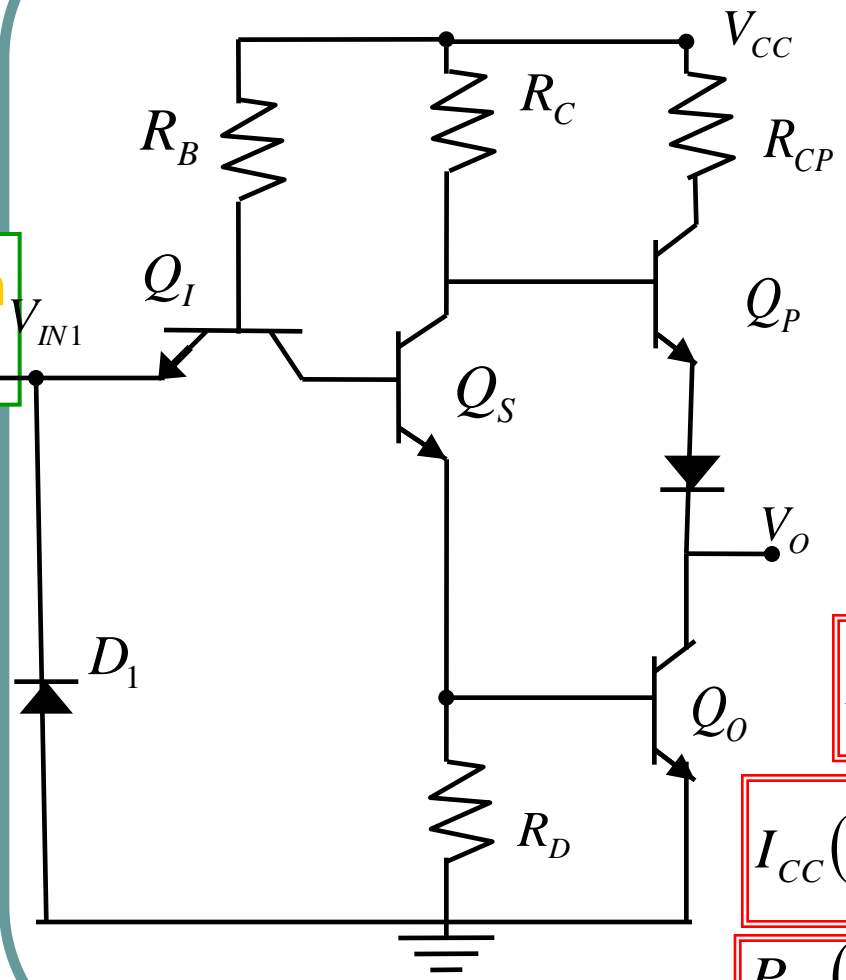

• Previous example

$R_B=4k\Omega, R_C=1.6k\Omega,$
 $R_{CP}=100\Omega, R_D=1k\Omega$

$$P_{CC}(avg) = 10.44mW$$

 

• Example


$R_B=40k\Omega, R_C=20k\Omega,$
 $R_{CP}=500\Omega, R_D=12k\Omega$

$$I_{CC}(OH) = I_{RB} = \frac{5 - 0.8 - 0.2}{40} = 0.1mA$$

$$I_{CC}(OL) = \frac{5 - 0.2 - 0.8}{20} + \frac{5 - 0.7 - 1.6}{40} = 0.268mA$$


$$P_{CC}(avg) = 0.5 \times 0.368 \times 5 = 0.919mW$$

High Speed TTL (HTTL)

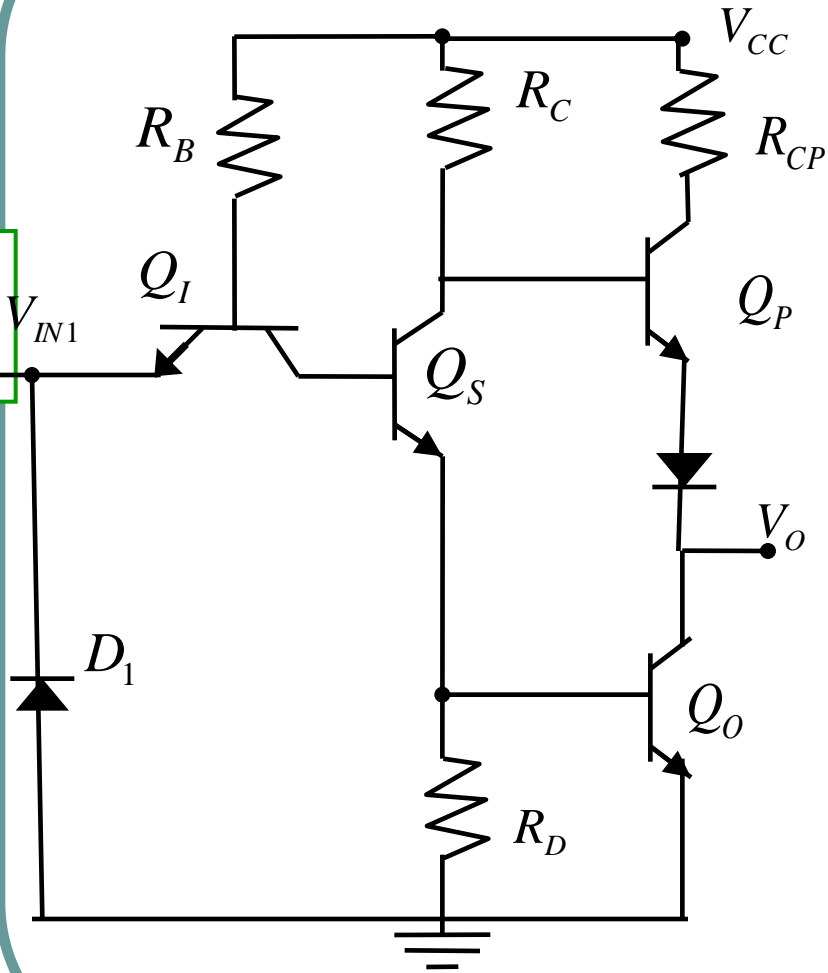



- Using smaller resistances increases the switching speeds

High Speed TTL (HTTL)

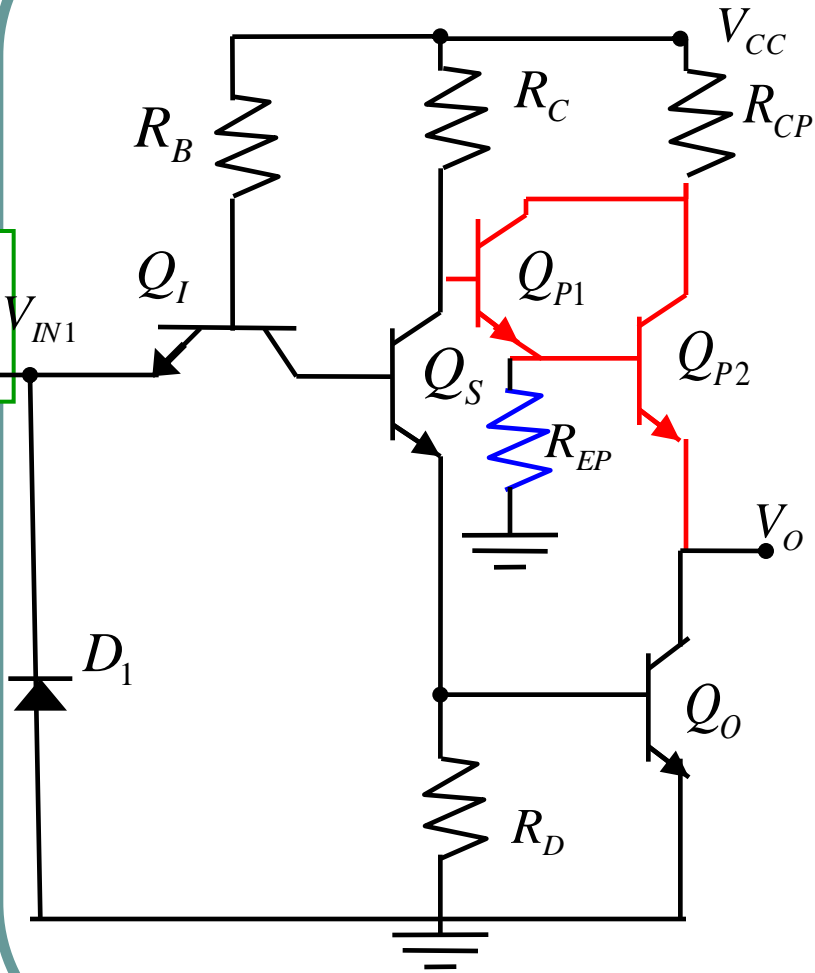

- Using smaller resistances increases the switching speeds
- Using **Darlington pair** (Q_{P1} , Q_{P2}) instead of Q_P increases the charging current of the load capacitance
- R_{EP} is used as a discharge path for the base of Q_{P2} .

High Speed TTL (HTTL)

 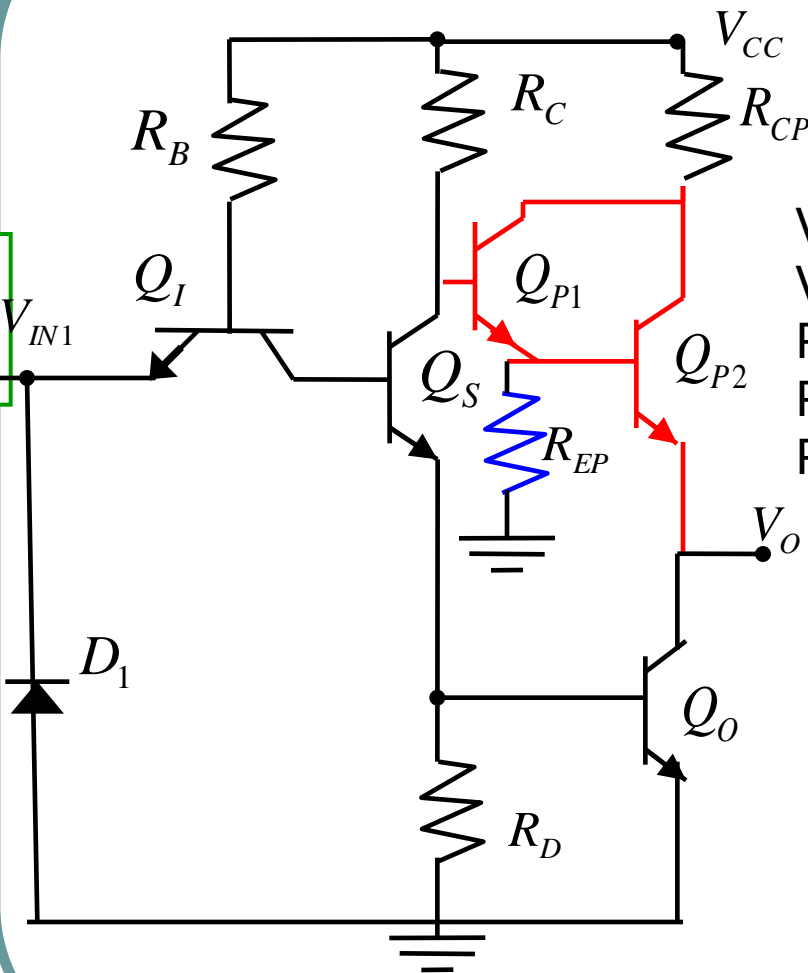

● Example (Prob. 7.18)

Plot the VTC of the HTTL circuits assuming:

- $V_{CE}(\text{sat})=0.2\text{V}$, $V_{BE}(\text{FA})=V_{BC}(\text{RA})=0.7\text{V}$,
- $V_{BE}(\text{sat})=0.8\text{V}$, $V_{CC}=5\text{V}$,
- $R_B=2.8\text{k}\Omega$, $R_C=760\Omega$, $R_{CP}=58\Omega$,
- $R_{EP}=4\text{k}\Omega$,
- $R_D=470\Omega$, and $\beta_F=70$.

● Solution

Refer to lecture class

- HW #7: Solve Problems: 7.1 , 7.5, 7.6, 7.9, 7.11, and 7.12

