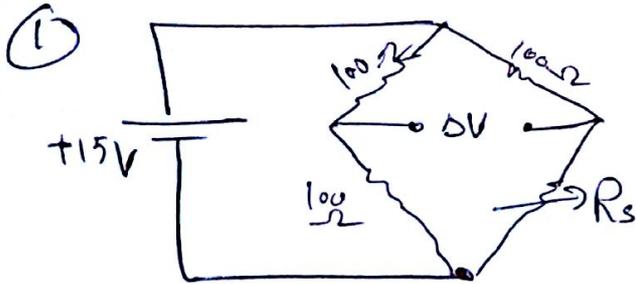


A wheatstone Bridge with $R_1 = R_2 = R_3 = 100 \Omega$. The sensor ($R_4 \equiv R_s$) has a nominal resistance of 100Ω . $V_s = 15 \text{ V}$.

- 1) Draw a schematic figure of the above measurement system.
- 2) If $R_s = 105 \Omega$, what is voltage offset (ΔV)?
- 3) If $\Delta V = 0.05 \text{ V}$, what is the value of R_4 ?
- 4) If $\Delta V = 0.06 \text{ V}$, what is the value of R_4 ?
- 5) What is the resolution of the bridge if ΔV jumps from 0.05 V to 0.06 V ? (i.e., the detector resolution is 0.01 V and use the above two points)?



②
$$\Delta V = 15 \left[\frac{100}{100+100} - \frac{105}{105+100} \right] = -0.183 \text{ V}$$

③
$$0.05 = 15 \left[\frac{100}{100+100} - \frac{R_{s,1}}{R_{s,1}+100} \right] \Rightarrow R_{s,1} = \overset{98.675}{\cancel{98.807}} \Omega$$

④
$$0.06 = 15 \left[\frac{100}{100+100} - \frac{R_{s,2}}{R_{s,2}+100} \right] \Rightarrow R_{s,2} = 98.413 \Omega$$


⑤ Resolution = $|DR_s| = \left| \frac{98.675}{\cancel{98.807}} - 98.413 \right|$

$= 0.394 \Omega$

$= 0.262 \Omega$

A wheatstone Bridge with $R_1 = R_2 = R_3 = 100 \Omega$. The sensor ($R_4 \equiv R_s$) has a nominal resistance of 100Ω . $V_s = 10 \text{ V}$.

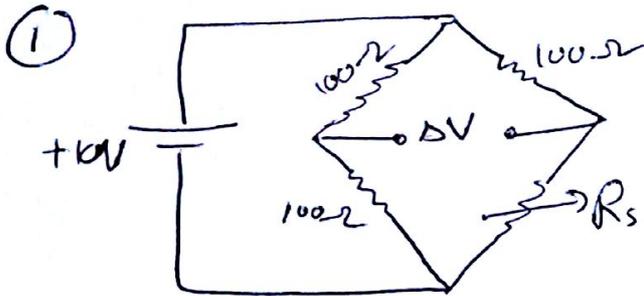- 1) Draw a schematic figure of the above measurement system.
- 2) If $R_s = 105 \Omega$, what is voltage offset (ΔV)?
- 3) If $\Delta V = 0.05 \text{ V}$, what is the value of R_4 ?
- 4) If $\Delta V = 0.06 \text{ V}$, what is the value of R_4 ?
- 5) What is the resolution of the bridge if ΔV jumps from 0.05 V to 0.06 V ? (i.e., the detector resolution is 0.01 V and use the above two points)?



②

$$\Delta V = 10 \left[\frac{100}{100+100} - \frac{105}{105+100} \right] = -0.122 \text{ V}$$

③

$$0.05 = 10 \left[\frac{100}{100+100} - \frac{R_{s,1}}{R_{s,1}+100} \right] \Rightarrow R_{s,1} = 98.020 \Omega$$

④

$$0.06 = 10 \left[\frac{100}{100+100} - \frac{R_{s,2}}{R_{s,2}+100} \right] \Rightarrow R_{s,2} = 97.628 \Omega$$

⑤

$$\text{Resolution} = |\Delta R_s| = |98.020 - 97.628|$$

$$= 0.392 \Omega$$