



Note: All resistances are in ohms.

Q1) (4 points) For the circuit shown in figure 1, use superposition principle to find the current I_x .

Q2) (5 Points) for the circuit shown in figure 2-a if the current $I(t)$ is shown in figure 2-b and $V(0)=0$, answer the following:

- find the equivalent capacitance as seen by the current source.
- find and plot $V(t)$ (the voltage across the current source).
- find $V(1.5 \text{ ms})$.

Q3) (7 points) for the circuit shown in Figure 3-a answer the following questions:

- Find the Thevenin voltage and resistance as seen by the load.
- Find the Norton current and resistance as seen by the load.
- Assume the load is varying resistance; what is the maximum power delivered to the load.
- Now assume that the load is **Non-linear circuit element** with I-V characteristic curve shown in **fig. 3-b**; plot the D.C.L.L and determine the current and the voltage of the load **graphically**.

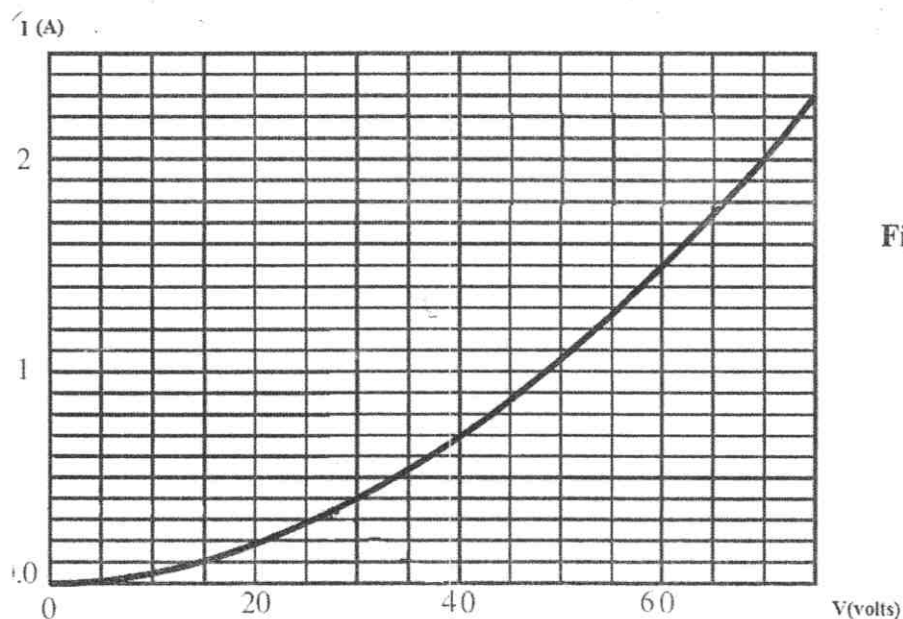


Fig. 3-b

Q4) (4 points) for the circuit shown in figure 4, answer the following questions:

- The impedance as seen by the source.
- $I_L(t)$, $V_L(t)$
- The phase difference between I and V .

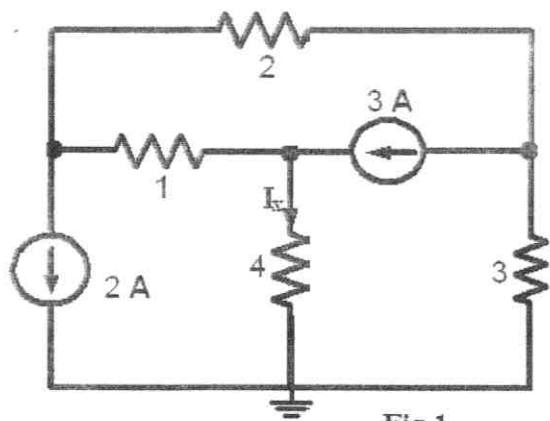


Fig 1

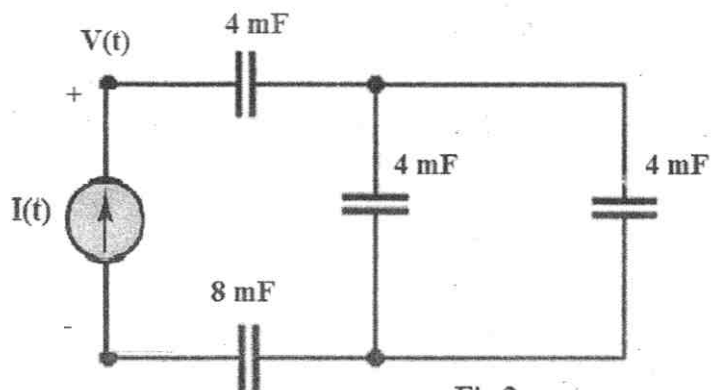


Fig 2-a

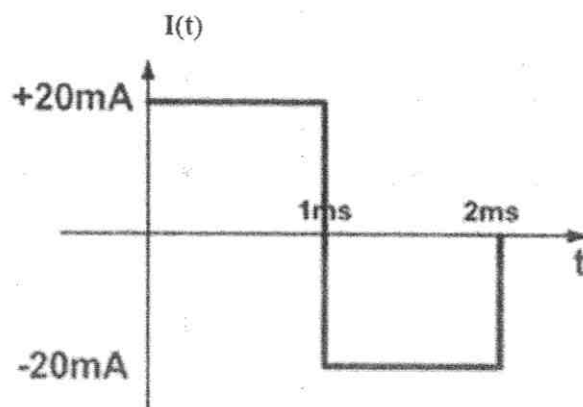


Fig. 2-b

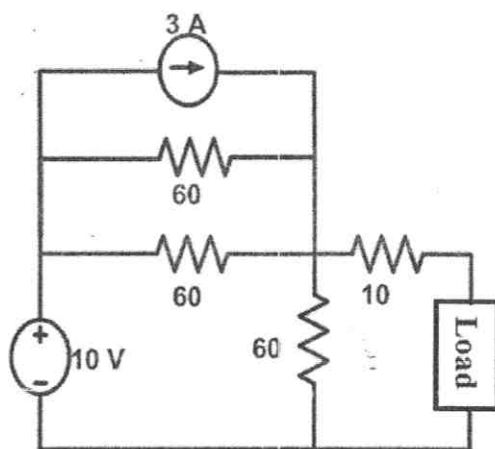


Fig 3-a


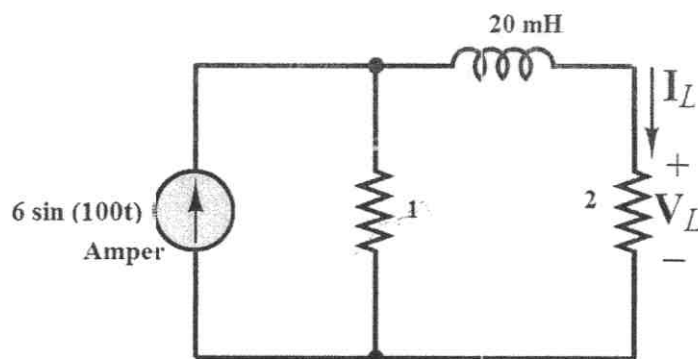
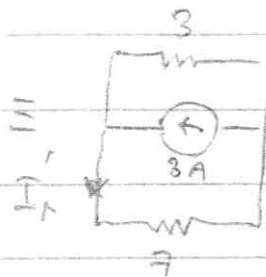


Fig. 4

Q1



$$I_x = I_x' + I_x''$$

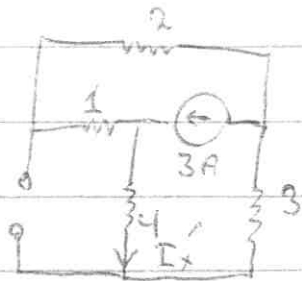

$$\Rightarrow I_x' = \frac{3/7}{7} \quad (3)$$

(Current Divider)

$$I_x' = 0.9 \text{ A}$$

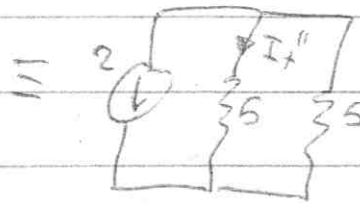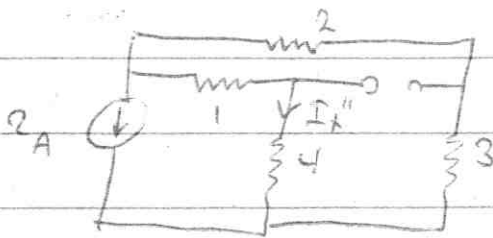


$$I_x'' = -1 \text{ A}$$

(Current Divider)

$$I_x = I_x' + I_x'' = -1 + 0.9 = -0.1 \text{ A}$$

Q2

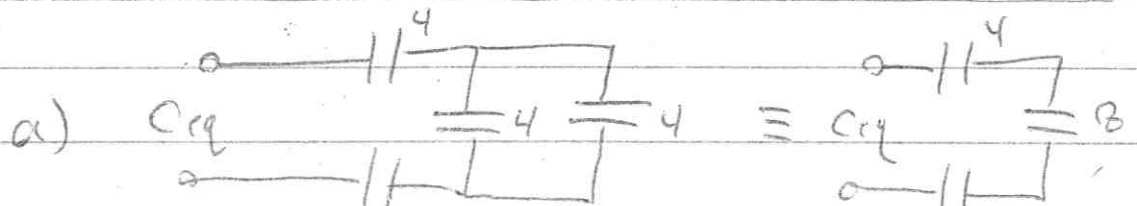

$$\frac{1}{C_{eq}} = \frac{1}{4} + \frac{1}{8} + \frac{1}{8} = \frac{4}{8}$$

$$\Rightarrow C_{eq} = 2 \text{ mF}$$

b) $V(0) = 0$

$$0 < t \leq 1 \text{ ms} \Rightarrow V(t) = V(0) + \frac{1}{C_{eq}} \int_0^t I(t) dt = \frac{1}{2(10)^{-3}} \int_0^t 20(10)^{-3} dt$$

$$= 10t$$

$$1 \text{ ms} < t < 2 \text{ ms} \Rightarrow V(t) = V(1) + \frac{1}{C_{eq}} \int_1^t -20(10)^{-3} dt$$

$$V(1 \text{ ms}) = 10(10)^{-3} \text{ V}$$


$$\Rightarrow V(t) = 20(10)^{-3} - 10t \text{ Volt}$$

$$1 \text{ ms} < t \Rightarrow V(t) = V(2 \text{ ms}) + \frac{1}{C_{eq}} \int_2^t I(t) dt$$

$$= 0$$



c) $V(1.5 \text{ ms}) = V(0) + \frac{1}{C} \int_0^{1.5} 20(10)^{-3} dt + \frac{1}{C} \int_{1.5}^{1.5} -20(10)^{-3} dt$

$$= 5 \text{ mV}$$

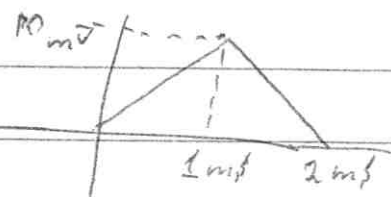

23


(a)

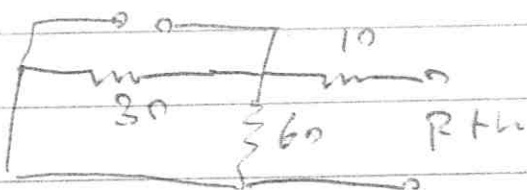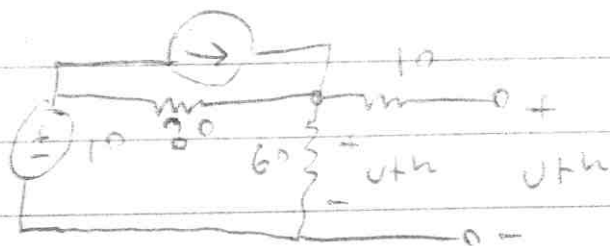

$$+8 - \frac{V_{th}}{60} - \frac{V_{th} - 10}{30} = 0$$

$$\Rightarrow V_{th} = 66.67 \text{ V}$$

$$R_{th} = (30 // 60) + 10 = 30 \Omega$$

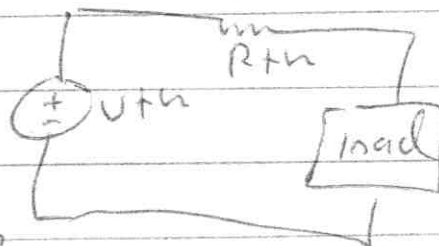


(b) $I_N = \frac{V_{th}}{R_{th}} = \frac{66.67}{30} = 2.23 \text{ A}$

$$R_N = R_{th} = 30 \Omega$$

(c) $P_{max} = \frac{V_{th}^2}{4 R_{th}}$

$$= 37 \text{ W}$$

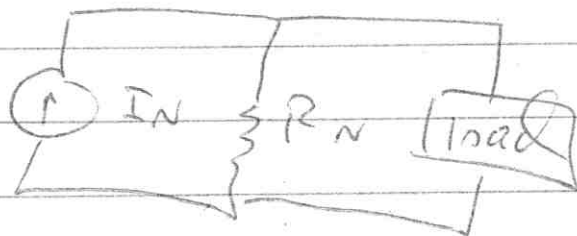


(d)

D.C.L.L equation:

$$-V_{th} + R_{th} I_x + V_x = 0 \Rightarrow I_x = \frac{V_{th}}{R_{th}} - \frac{V_x}{R_{th}}$$

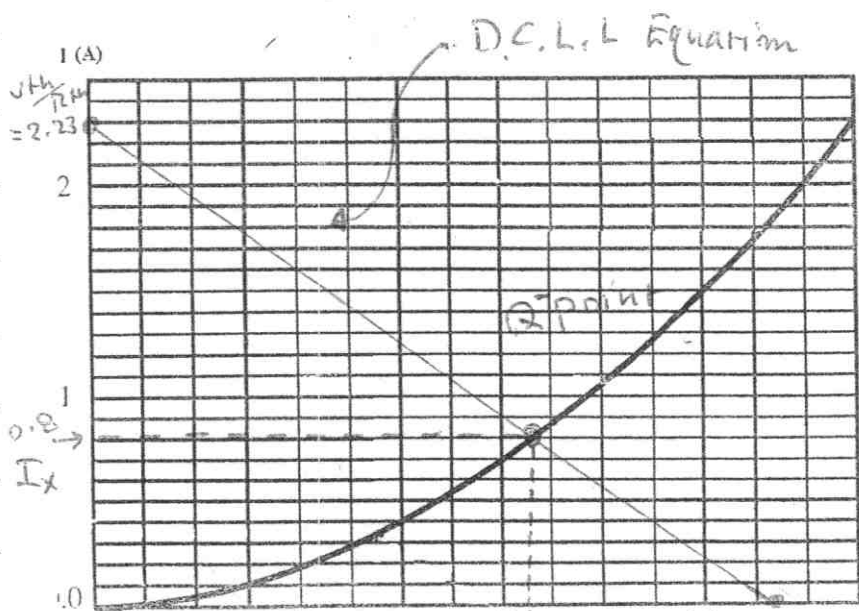
$$\Rightarrow I_x = 2.23 - \frac{V_x}{30}$$



Q4

$$\omega = 100$$

$$j\omega L = 2j$$

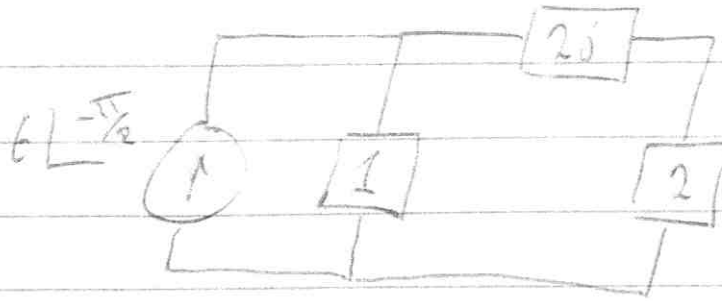

a) Impedance $Z_{eq} = 1 \parallel (2+2j) = \frac{2+2j}{3+3j} = 0.77 + 0.15j \equiv 0.78 \angle 11^\circ$

b) $\tilde{I}_L = 6 \angle -\frac{\pi}{2} \left[\frac{Z_{eq}}{2+2j} \right] = 1.67 \angle -123^\circ$

$$\Rightarrow I(t) = 1.67 \cos(100t - 123^\circ)$$

$$\tilde{V}_L = 2 \tilde{I}_L = 3.32 \angle -123^\circ$$

$$V_L(t) = 3.32 \cos(100t - 123^\circ)$$

c) Phase Difference between $\tilde{I}_L$ & $\tilde{V}_L$ is 0° .